

2/8/18.

Circuit Analysis.

PAGE NO.:

DATE: / /

1. Active Element: It is one which will possess energy of its own.
Ex: Voltage source, Current source.


2. Passive Element: It will take energy from another source Instantaneously
Ex: R, L, C.

⇒ Voltage source: { Either it can Ideal sources or Current source } practical sources.


⇒ Ideal sources: ① Dependent sources / Controlled sources.

② Independent sources.


D.V.S

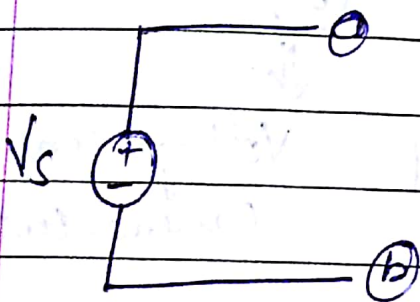


P.V.S.

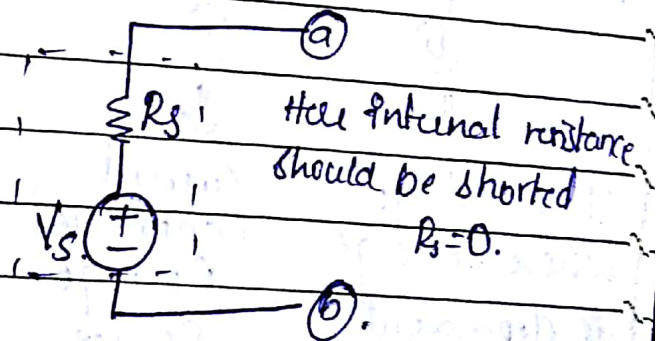

D.I.S

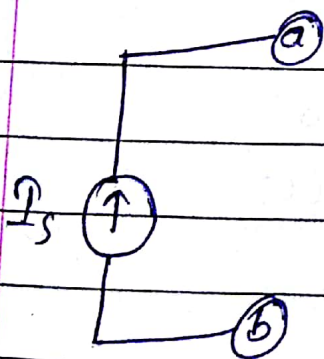

P.I.S

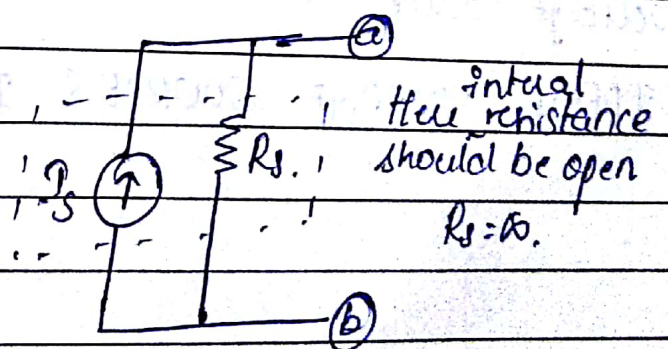


Independent Sources: Its value does not change with any V and I in ckt.

EX: Battery $\Rightarrow$ 

Dependent sources: Its value changes w.r. to change in V , I , in ckt.

Types of dependent sources:

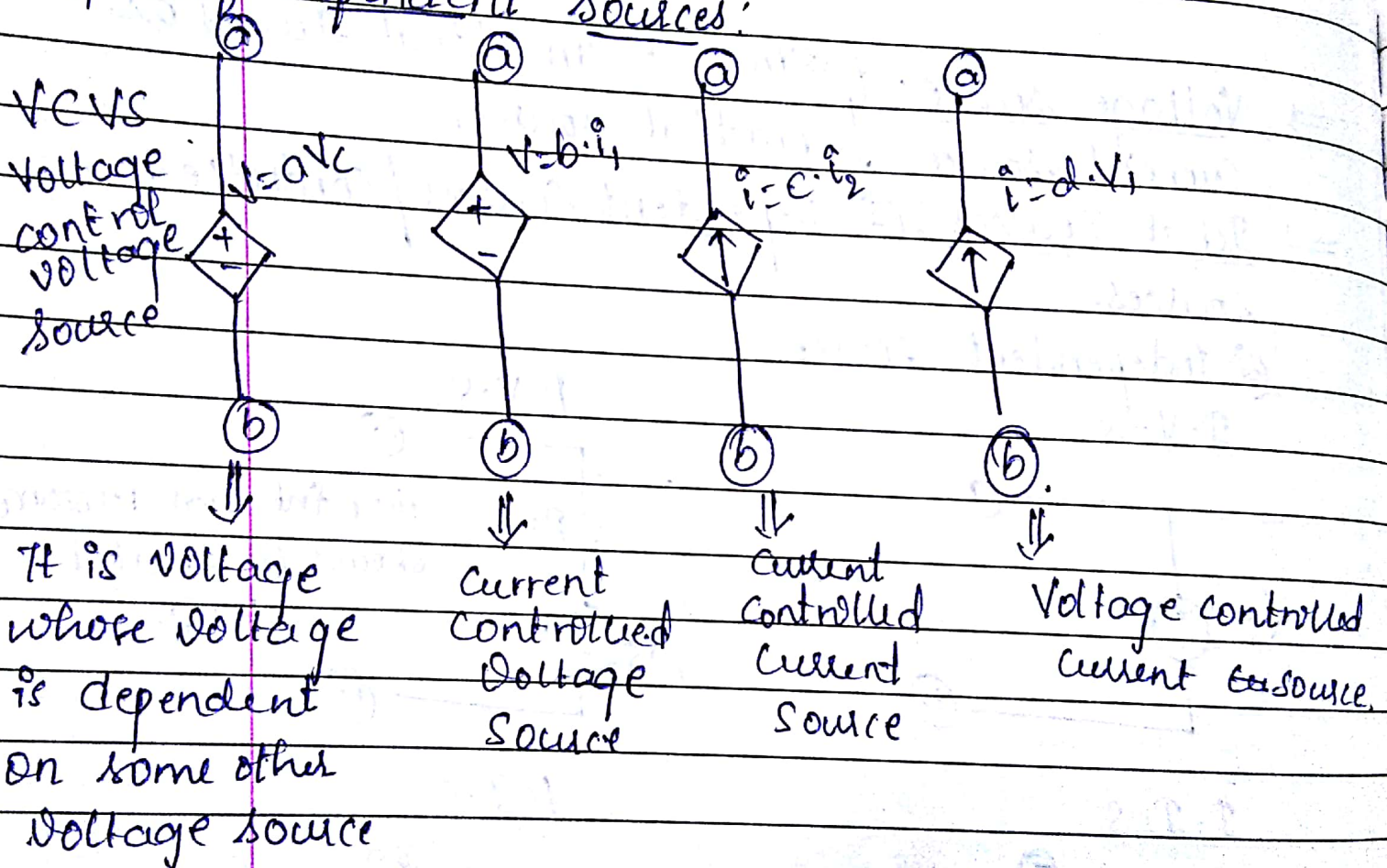

IDEAL VOLTAGE SOURCES IN SERIES:

"

"




"

"


PARALLEL:

I · V · S · S


PAGE NO. :
I · V · S · S · P.

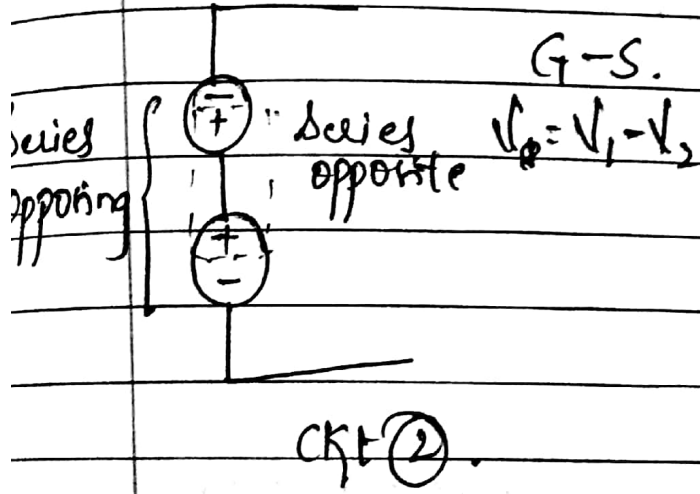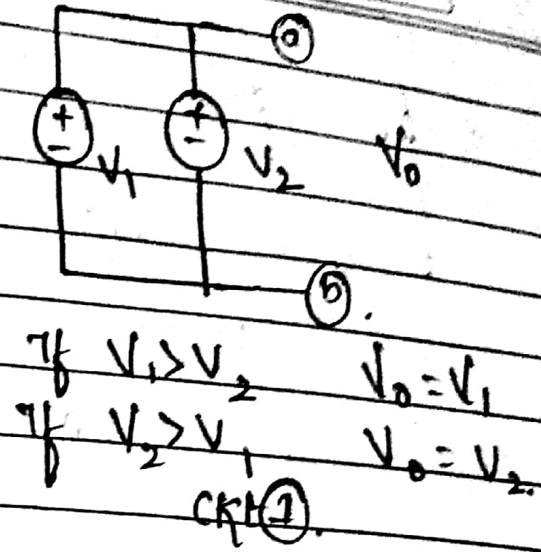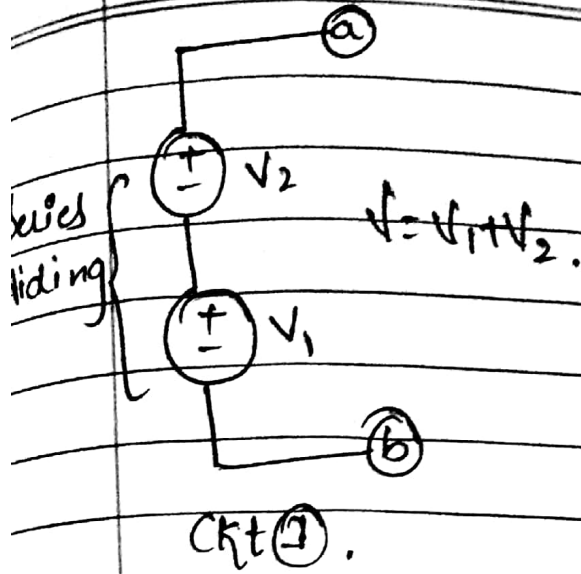


I · C · S · S

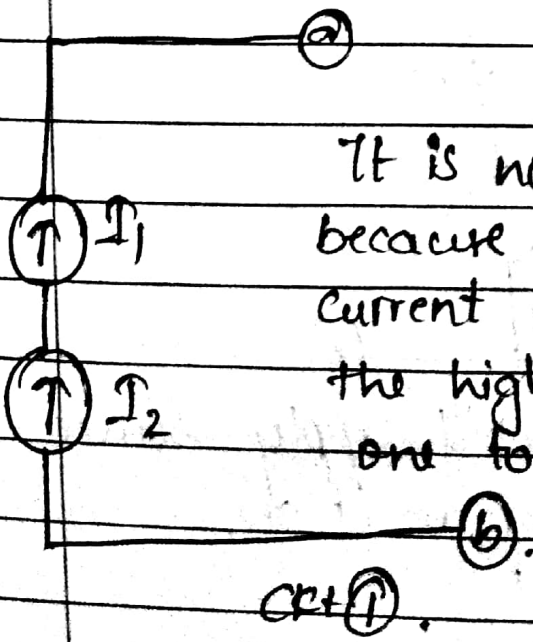

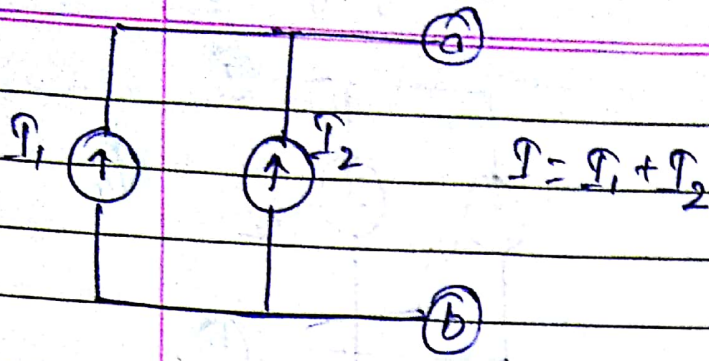It is no use because output current will be higher one, the higher one also drag lower one to that level. so no use



Ckt (2)


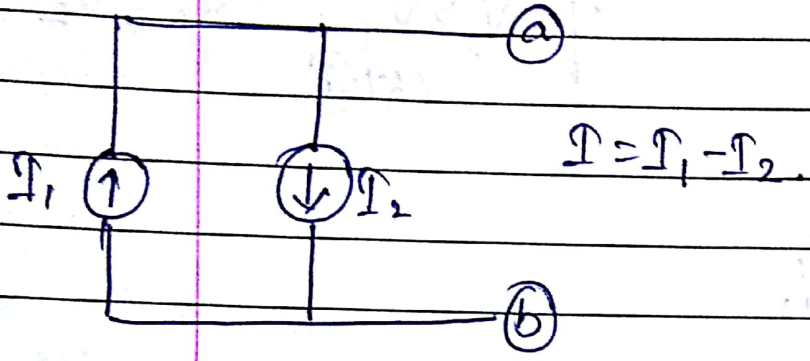


Ckt (3)

Practical Voltage sources.

P.V.S.S


P.V.S.P.(CS)

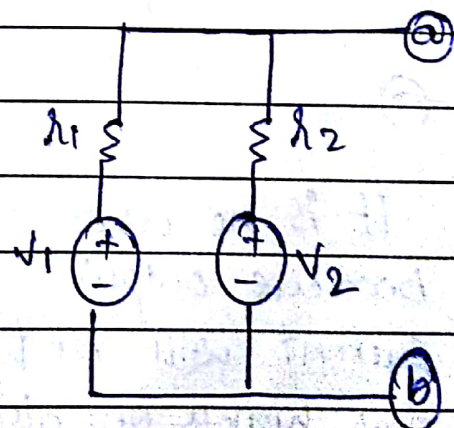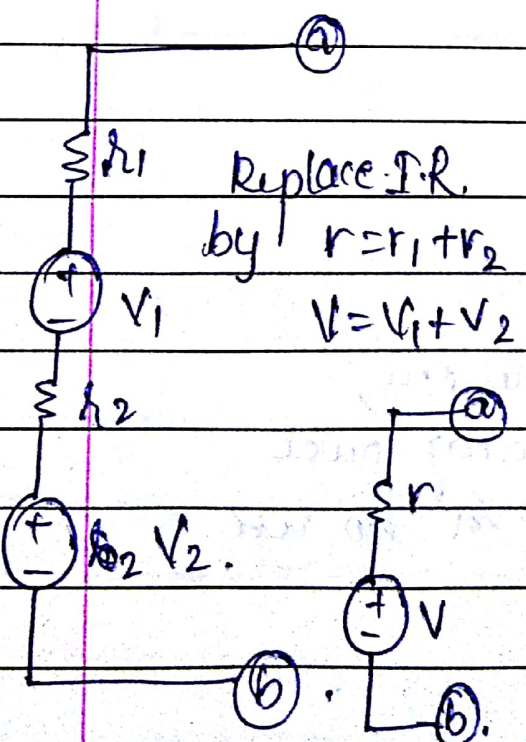


Here will apply source Transformation

P.V.S.P: To determine V_0 Source Transformⁿ Req^d.

P.D.S.S. (S2)

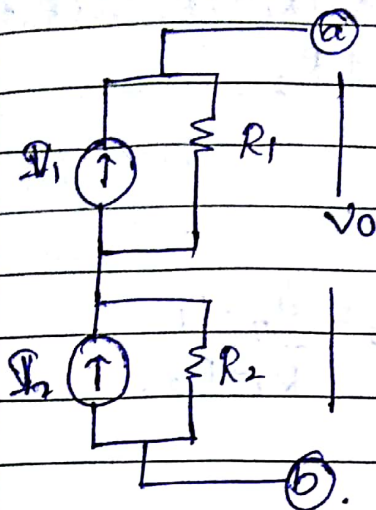


P.D.S.P.

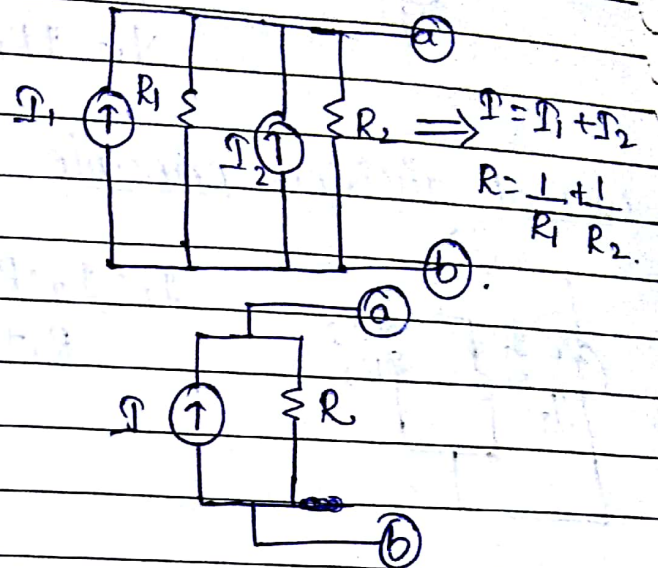


V_0 is obtained using Source Transformⁿ.

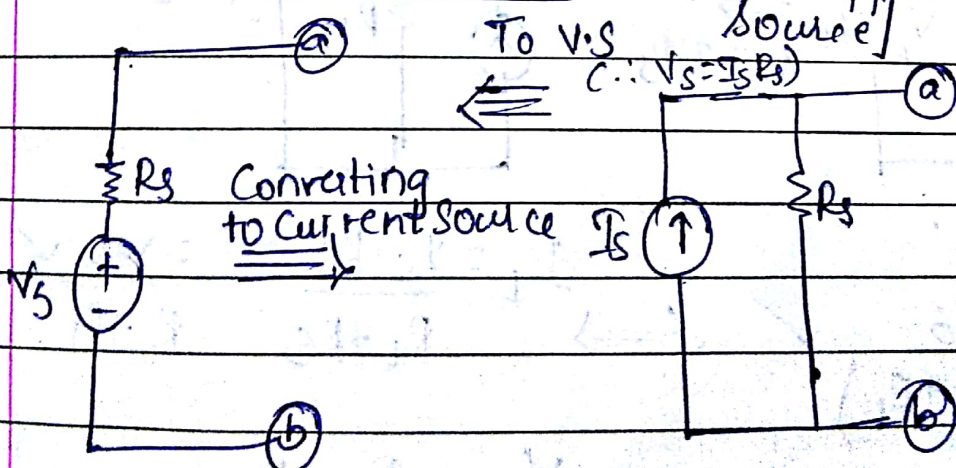SOURCE TRANSFORMATION: [It is applied only for practical source]



It is done only when


$$V_s = I_s R_s, \quad I_s = \frac{V_s}{R_s}$$

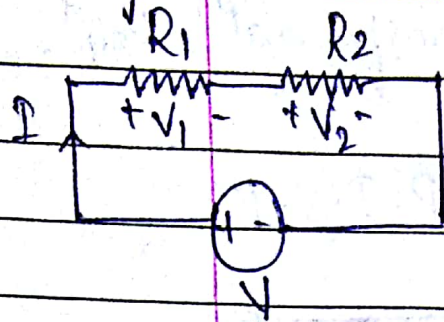Voltage Division principle.

Current flowing in both resistors is same as they are connected in series.


$$V = V_1 + V_2 \quad V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$V_1 = IR_1 \quad V_2 = IR_2$$

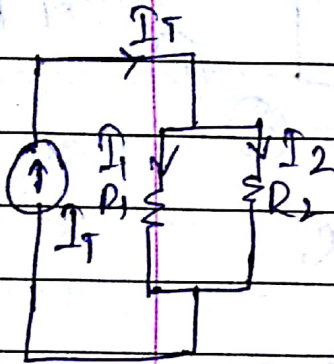
Current division principle

$$I_1 = \frac{I_T \cdot R_2}{R_1 + R_2}$$

$$I_2 = \frac{I_T \cdot R_1}{R_1 + R_2}$$

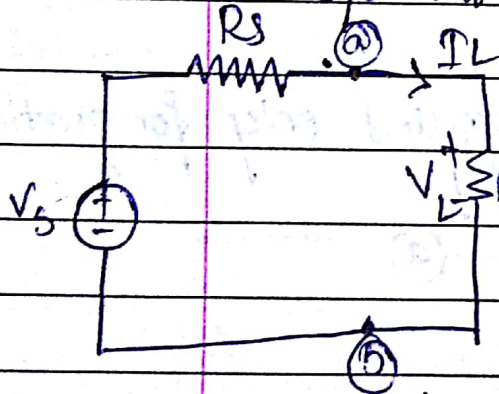Source Transformⁿ for closed ckt.

$$V_S = I_S R_S$$

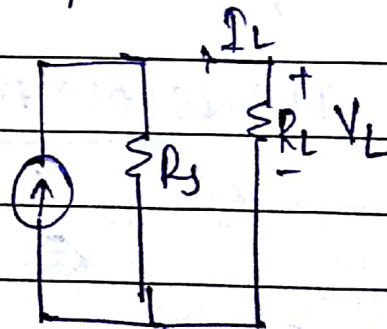

$$I_L = \frac{V_S}{R_S + R_L} \quad \checkmark$$

$$I_L = \frac{I_S \cdot R_S}{R_L + R_S} = \frac{V_S}{R_L + R_S} \quad \checkmark$$


$$V_L = I_L \cdot R_L$$

$$V_L = I_L R_L$$


Norton's Current Source in Series (S2)

Page No. 355

DATE: / /

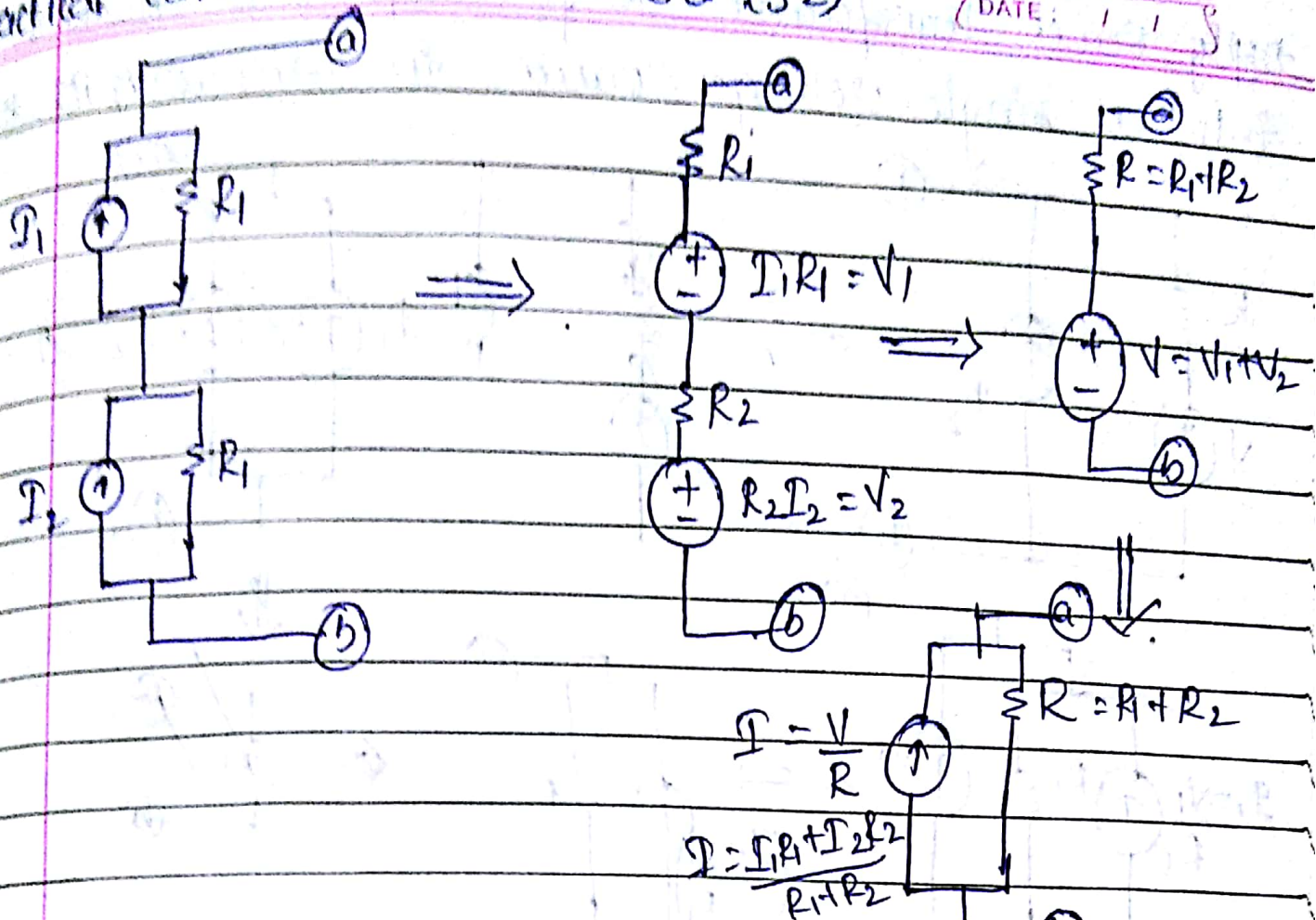




P.V.S.P.C.S2)

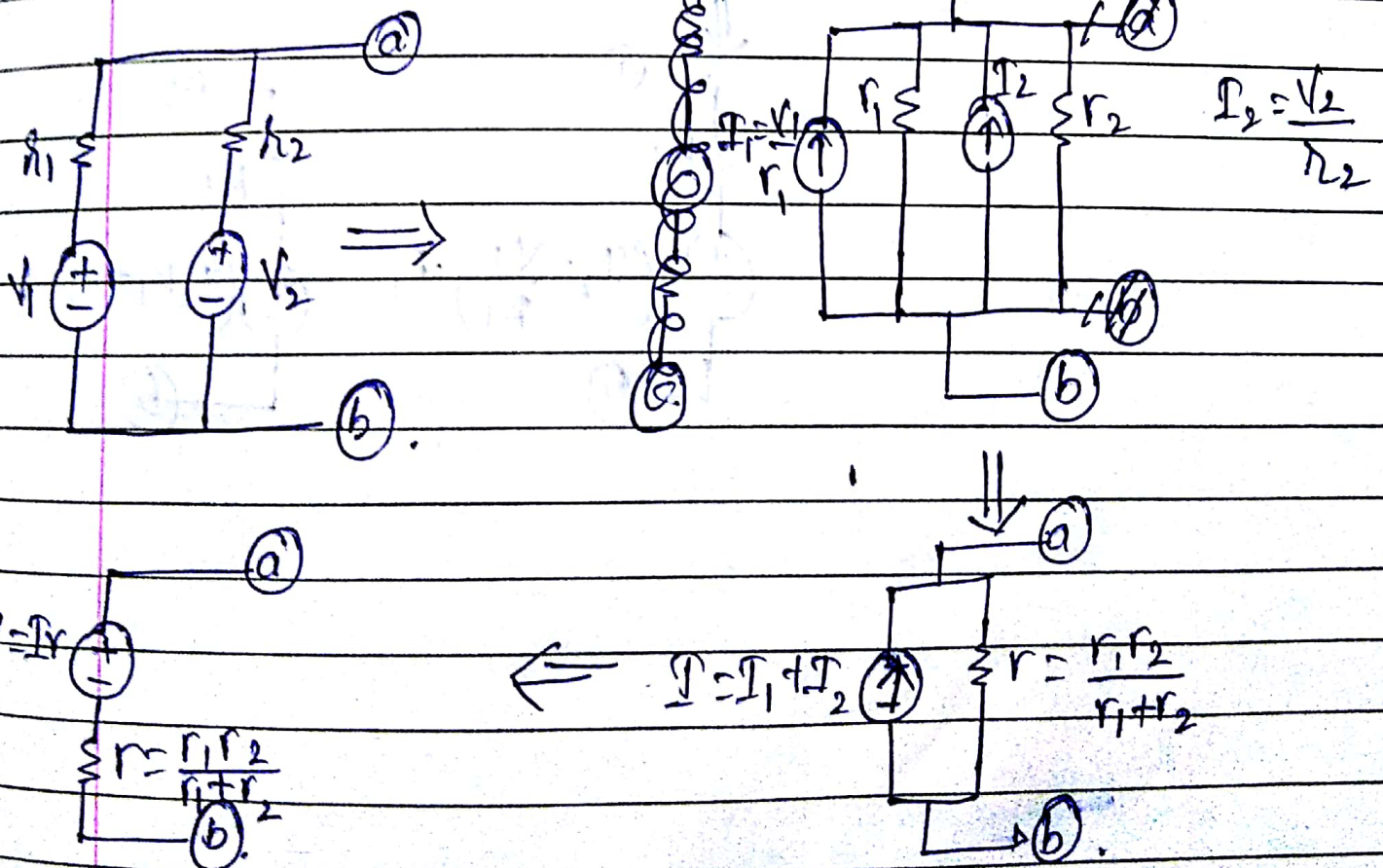

Nodal
 6Ω
 V_1
 $2V$

PAGE NO.:
 DATE:



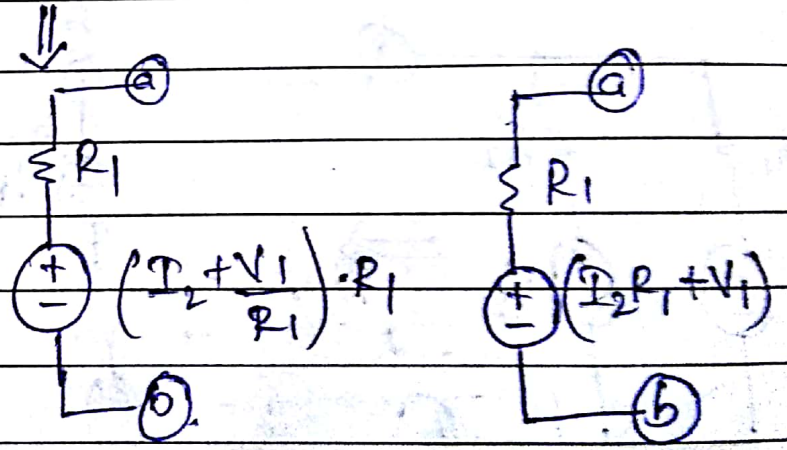
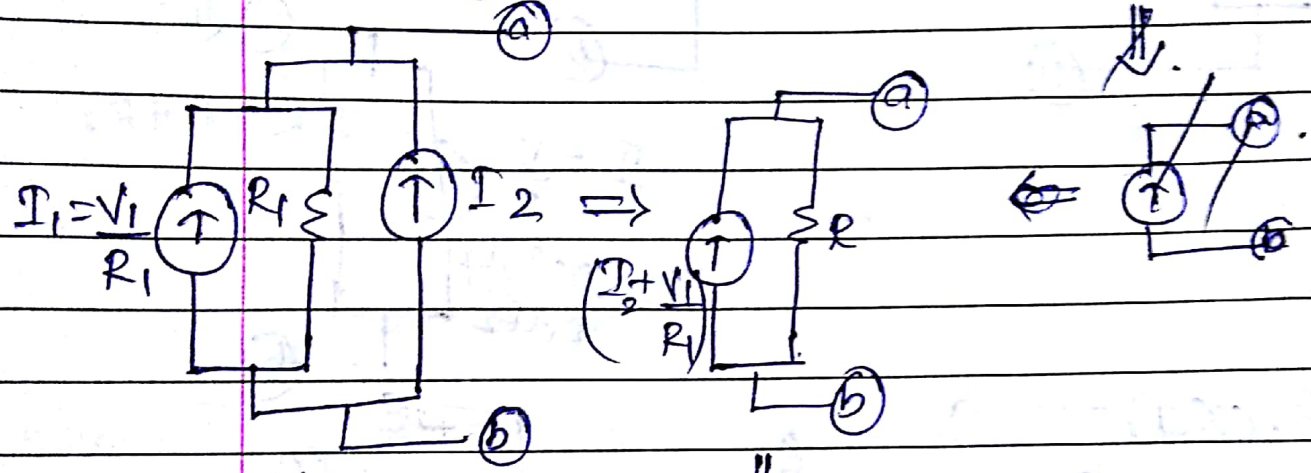
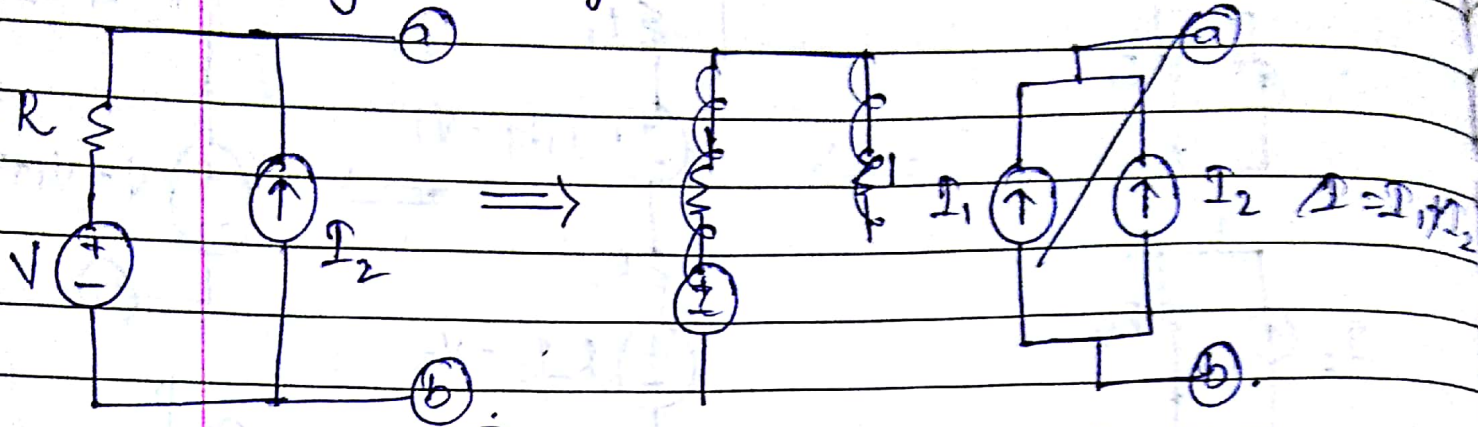
Apply Source Transformation to full ckt and convert this into a single voltage source in series with its r.



Q. Convert foll' ckt into a single voltage source using S.T

PAGE NO.:

DATE:

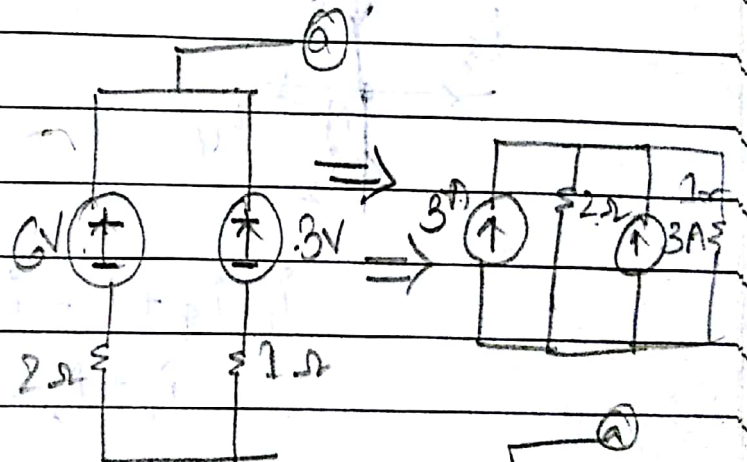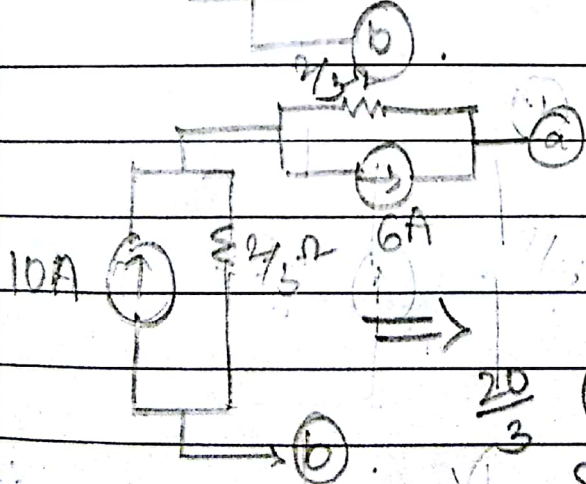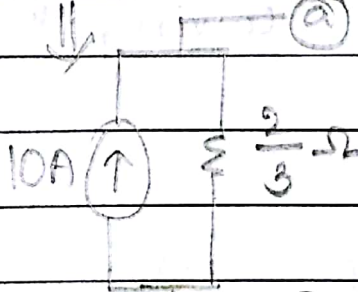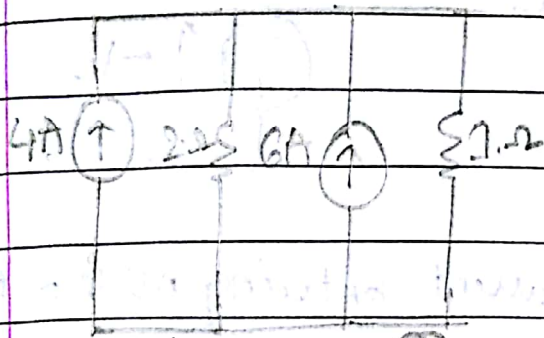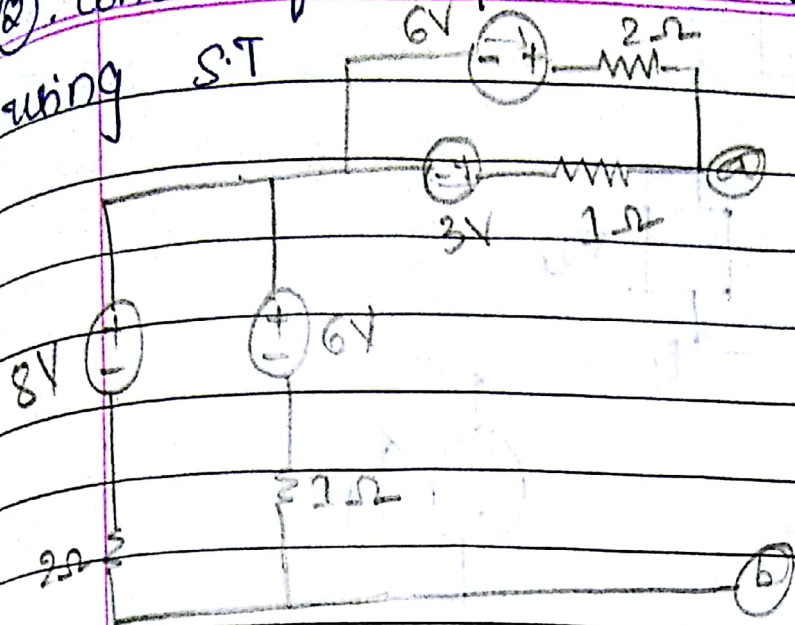

$$R = \frac{2}{3} + \frac{2}{3} = \frac{4}{3} \Omega$$


$$V = \frac{20}{3} + \frac{12}{3} = \frac{32}{3} \text{ V}$$

Analysis:


KVL and KCL

Current Entering = Current Leaving



PAGE NO. _____
DATE: / /

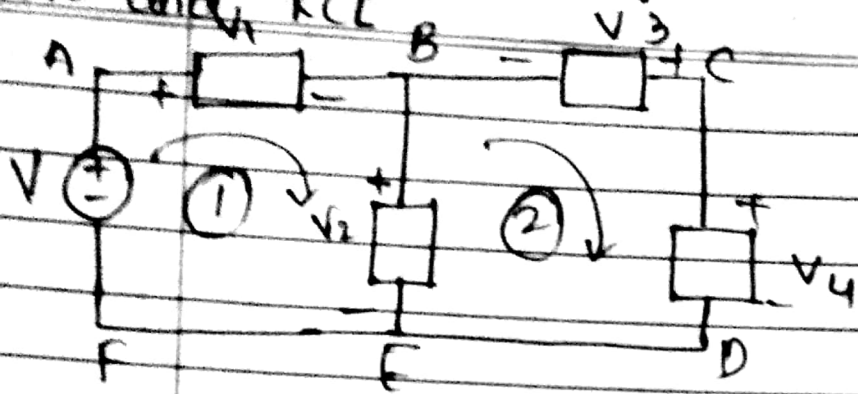

loop 1 $V - V_1 - V_2 = 0$

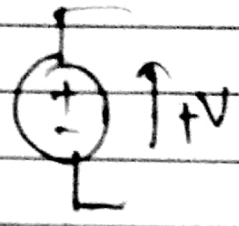

loop 2 $V_2 + V_3 - V_4 = 0$

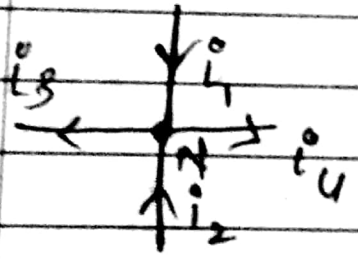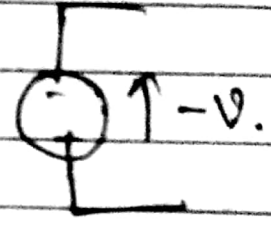

current Entering node = +I
leaving " = -I



$$i_1 - i_4 + i_2 - i_3 = 0$$

$$i_1 + i_2 = i_3 + i_4$$

Find the current I by reducing the ckt to the right side of terminals x, y to its simplest form using source transformation

PAGE NO.:

DATE:

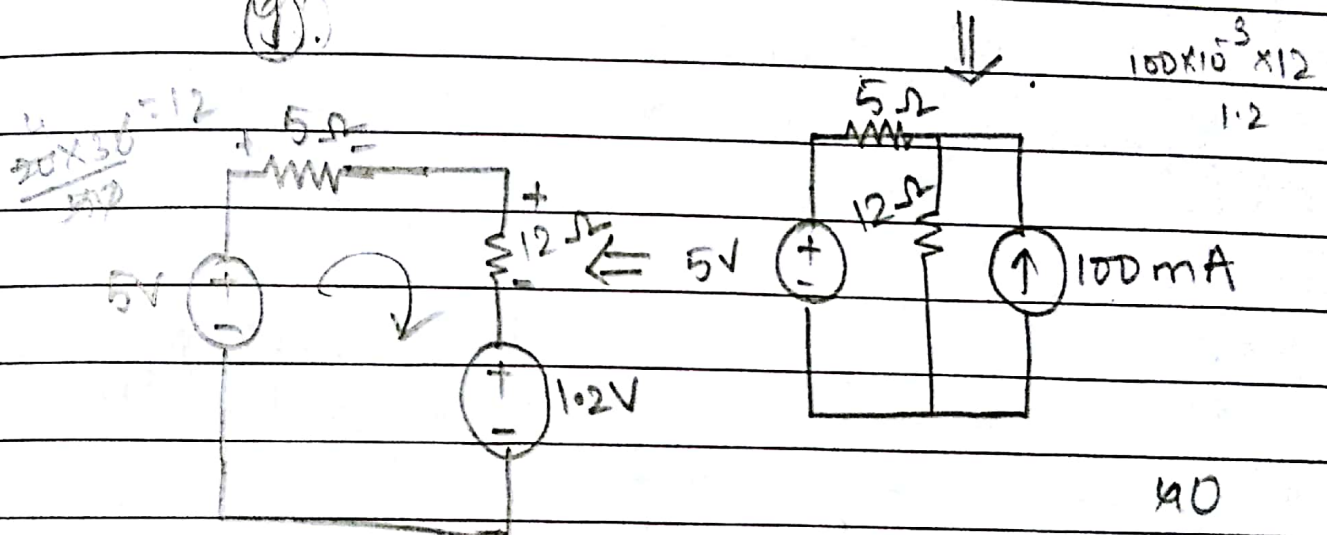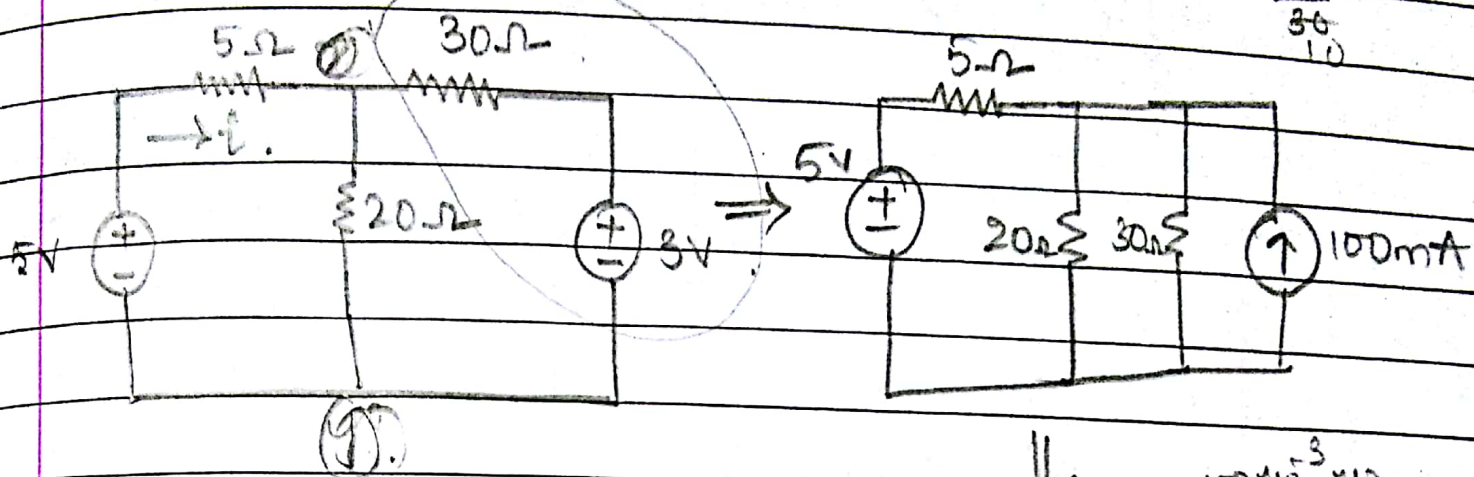

$$5 - 5i - 12i - 1.2 = 0.$$



$$3.8 = 17i$$

$$i = \frac{3.8}{17} = \frac{2.2}{17} \times 10^{-1} = 0.22A = 220mA.$$

without calc
0.2235A.

*. Determine current i_2 in the follⁿ ckt Wrong

S.T

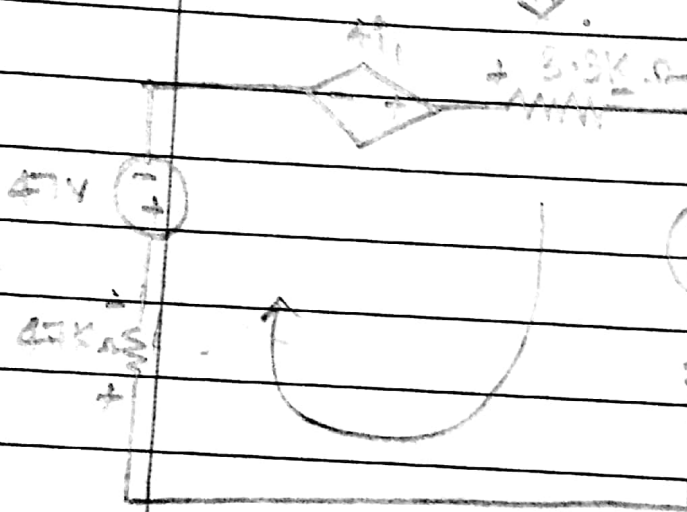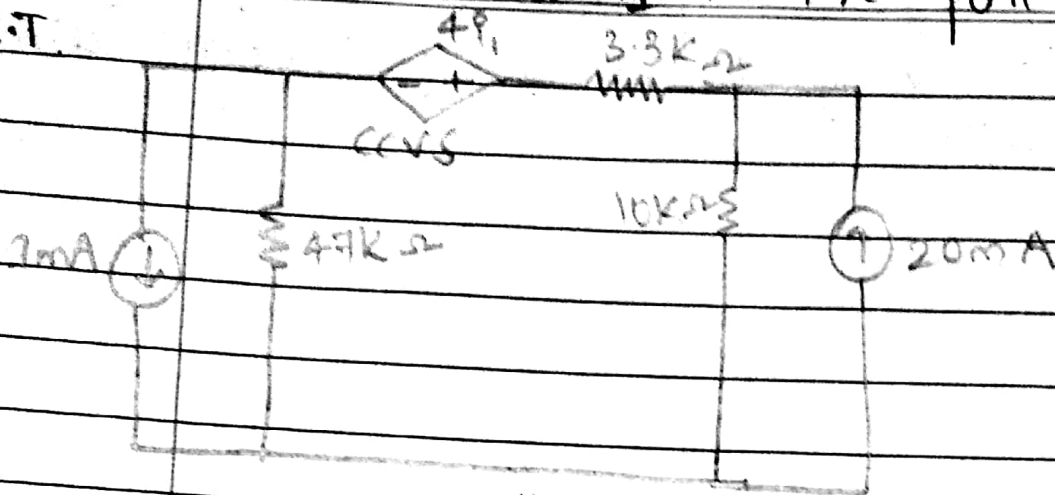

Current is flowing in opp
direction bec^z 200V
is max voltage
& flows from 200V to
lower potential.



$$-47K \times i_1 - 47 + 4i_1 - 3.3K i_1 - 200 - 10K i_1 = 0$$

$$(-47 + 3.3 - 10) i_1 + 4i_1 = 247$$

$$-60.3 \times 10^3 i_1 + 4i_1 = 247$$

$$i_1 = \frac{247}{60296} = -4.09 \text{ mA}$$

$$60296 \quad \text{or}$$


$$= 4.387 \text{ mA}$$

$$i_2 = -17.598 \text{ opposite direction}$$

$$\begin{array}{r} -43 \\ + 3.3 \\ \hline -56.3 \end{array}$$

$$503$$
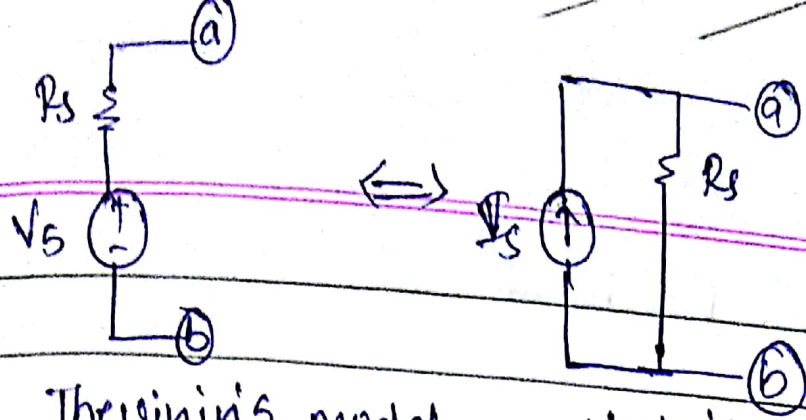
$$\begin{array}{r} 82 \\ 4.387 \times 4 \\ \hline 17.548 \end{array}$$



Thevenin's model

Norton's Equi model.

SOURCE SHIFTING When Ideal Sources are present in the network then source transformation cannot be done as these ideal sources will not be having internal resistance. In order to solve such problems source shifting method is used which is as shown below and there are two types of source shifting


(i) A Voltage source shift (V-Shift)
(ii) A Current " " (I-Shift)

Let us consider follⁿ examples.


$$I \rightarrow 0 \Rightarrow \text{O/C.}$$


$$V \rightarrow 0 \Rightarrow \text{S/C.}$$

Voltage source shifting



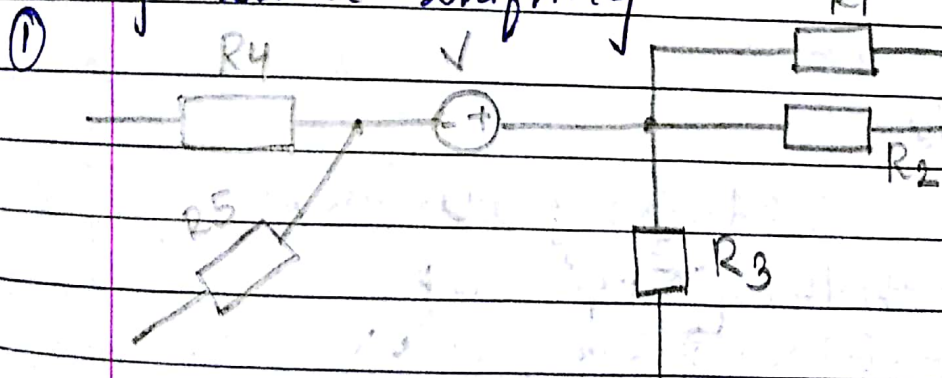


at a time one side is applied




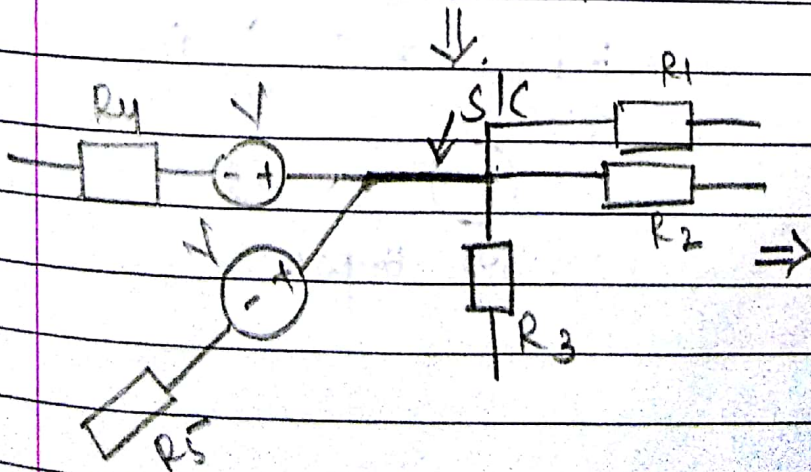


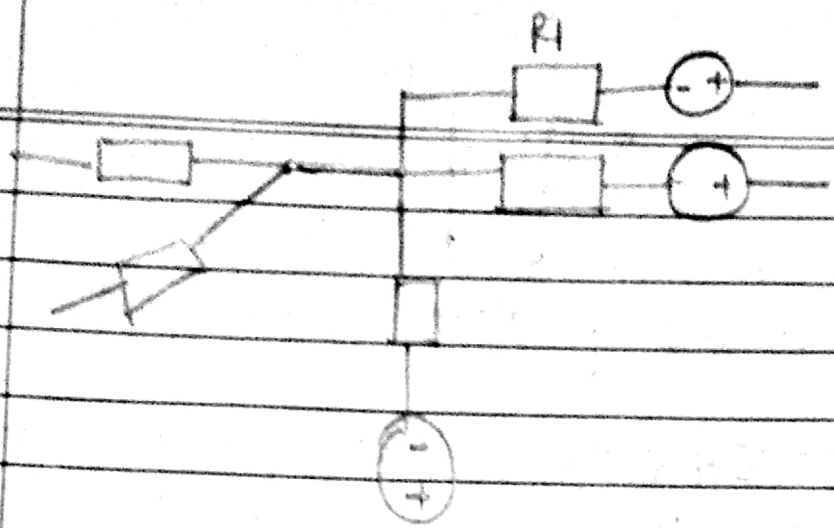

Current Source Shifting:

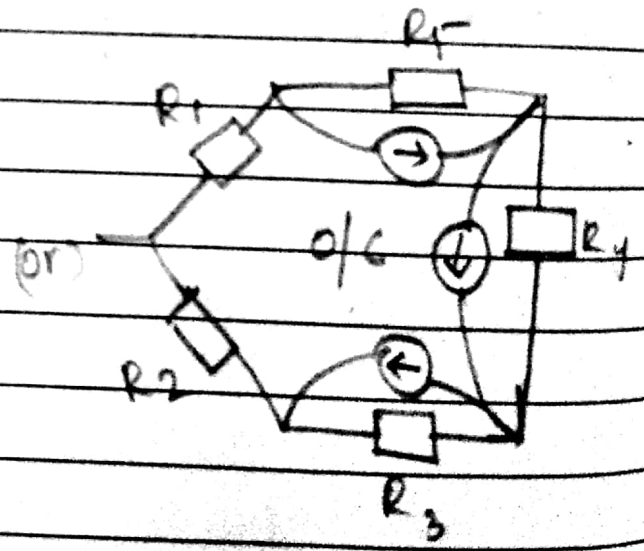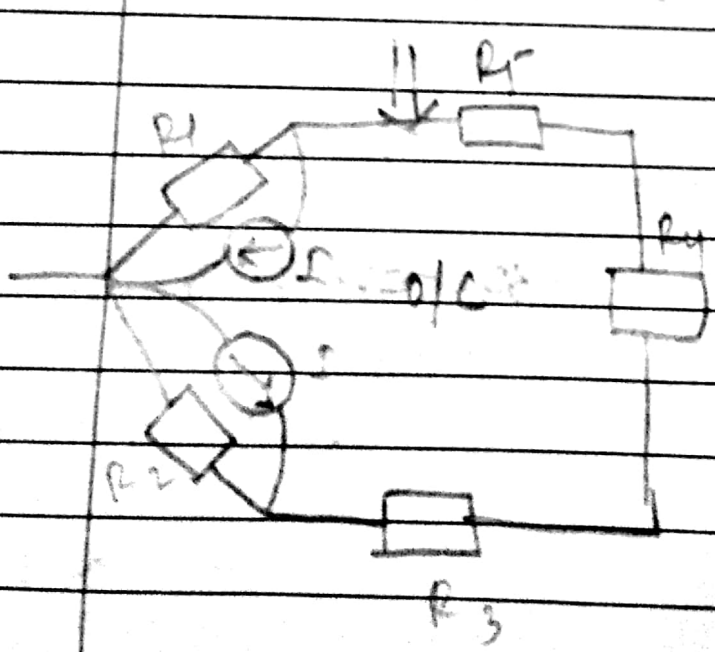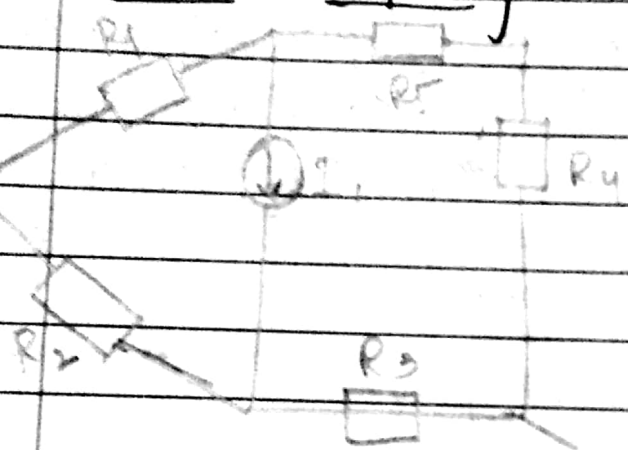

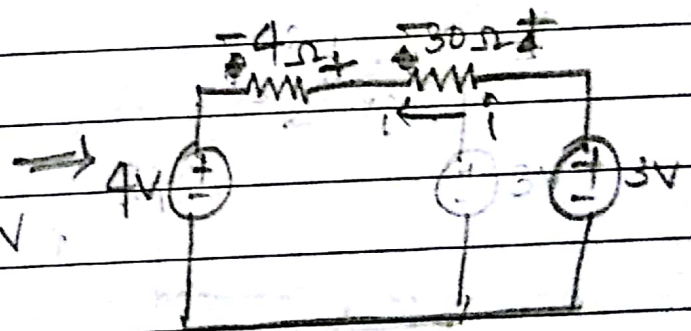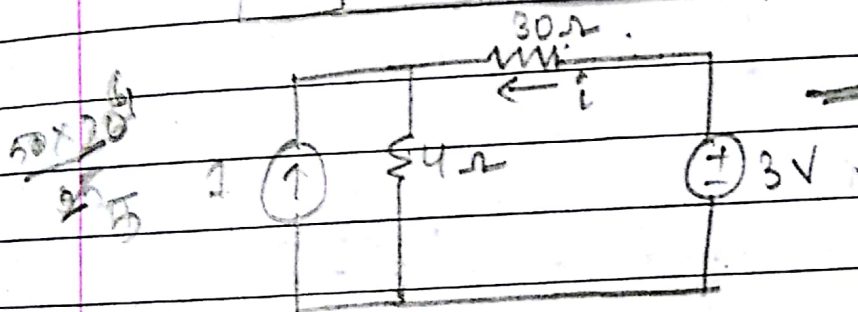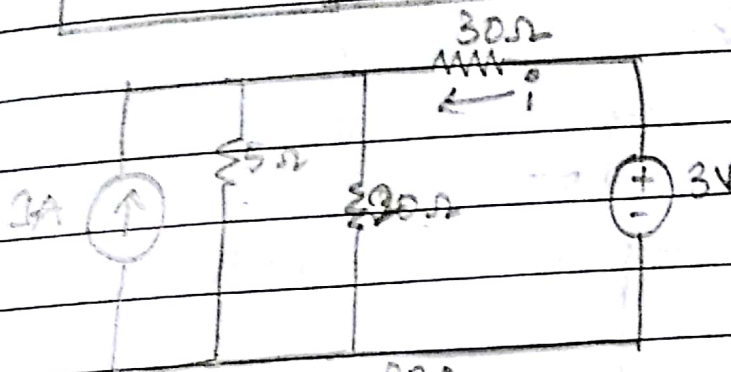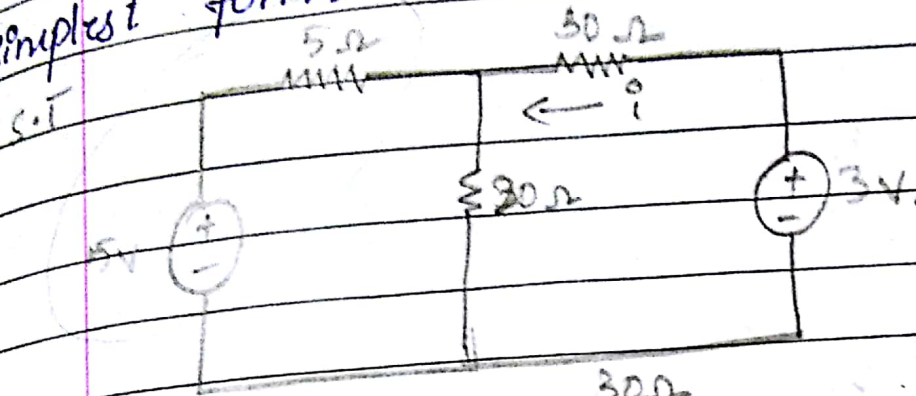Find current i in the follⁿ ckt using source transformation by reducing the follⁿ ckt into its simplest form



$$+30i - 4i - 4 + 3 = 0$$

$$26i = 1$$

$$i = 1/26$$

$$i = -29.41 \text{ mA}$$




Am Sai:

and Potentiometer:

PAGE NO.:

DATE:

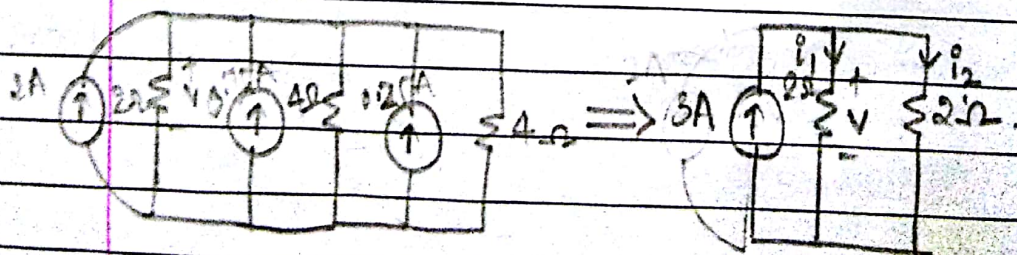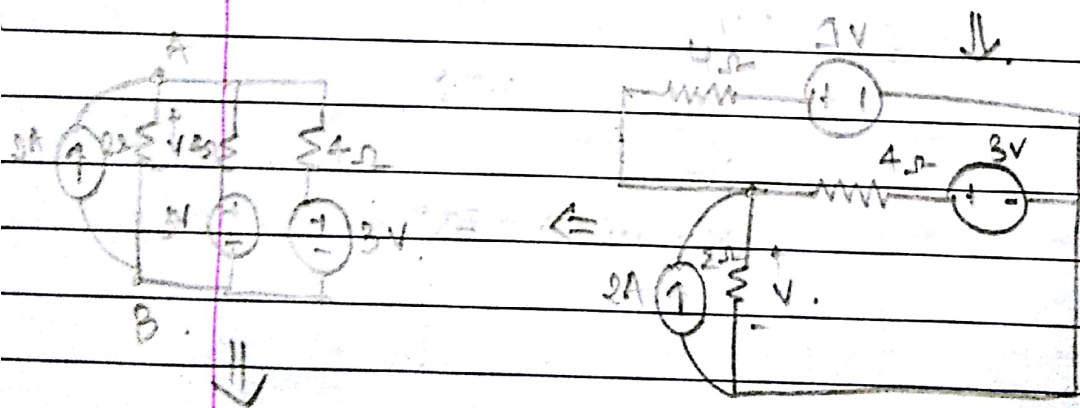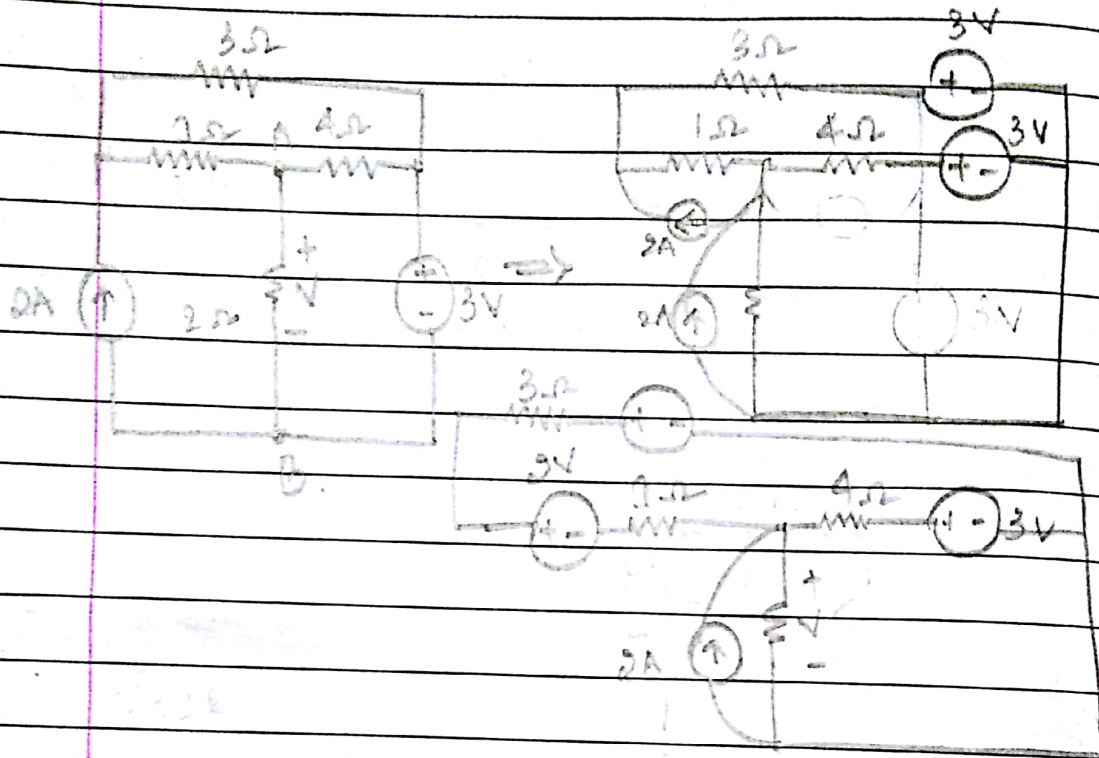⑤. Use source shifting and source transformation to determine the voltage across 2Ω resistor in the given ckt.



$$2 + 0.75 + 0.25 = 3A$$

$$\frac{2 \times 4}{8} = 2\Omega$$


current division principle. $P = 3$

same resistor $\therefore \frac{3}{2} = 1.5A = I_1 = I_2$

$$I_1 = \frac{I \times R_2}{R_1 + R_2}$$

$$I_1 = \frac{3 \times 2}{2 + 2} = \frac{6}{4} = 1.5A$$

$$V = I_1 \times 2 = 3V$$





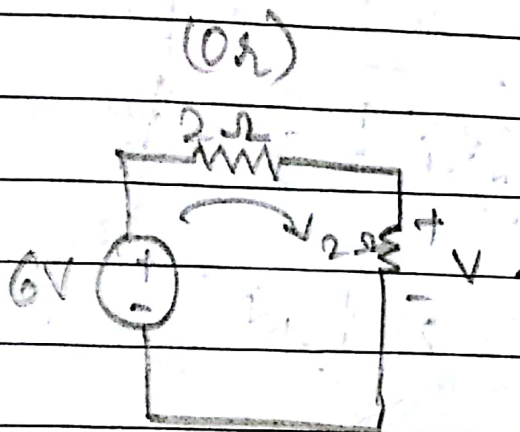


$$6 - I(4) = 0$$



$$I = \frac{6}{4} = 1.5A$$

$$V_1 = 1.5 \times 2 = 3V$$

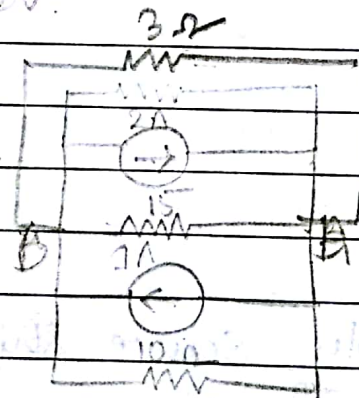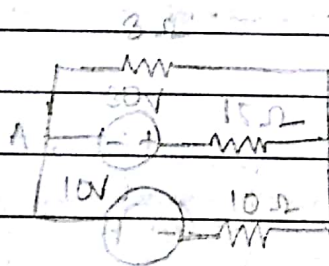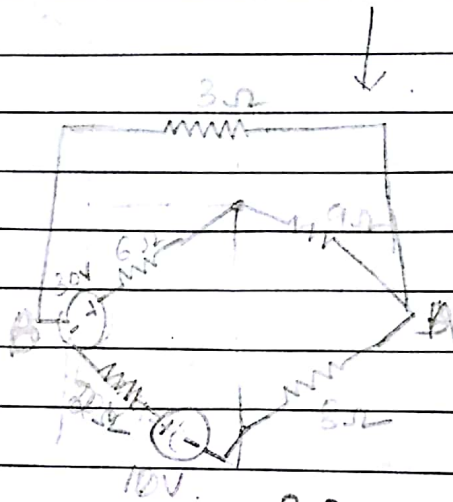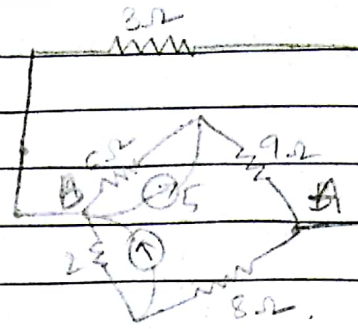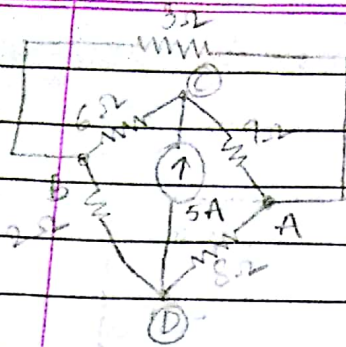5. Apply source shifting And source transformation for finding voltage V_{ab} in network.


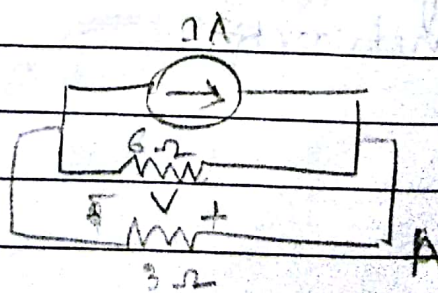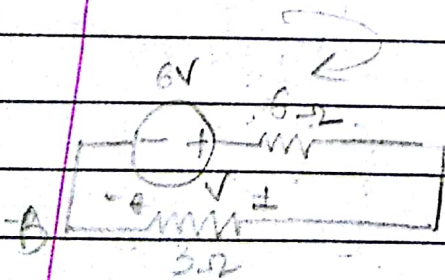
$$\begin{aligned} & 15 \times 62 \\ & \frac{25}{7} \end{aligned}$$



$$+6 \cdot 6\Omega + 3i = 0$$

$$6 = 9i$$






$$i = \frac{2}{3}$$

$$V = 2/3 \times 3 = 2V \quad -2V$$

PAGE NO.:

DATE: / /


$$V_{ba} = 2V \quad V_{ab} = -2V$$

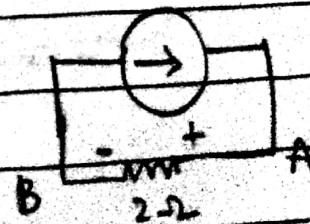
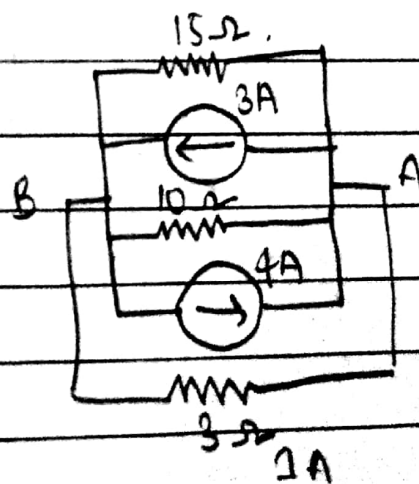
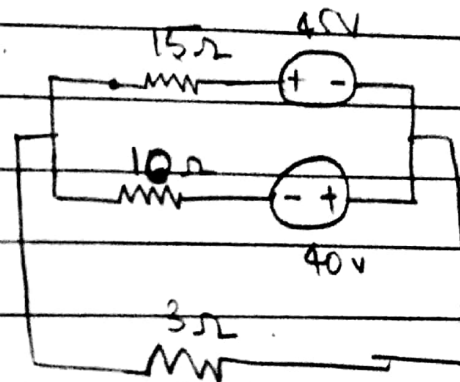
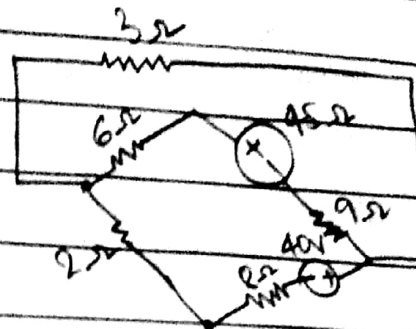
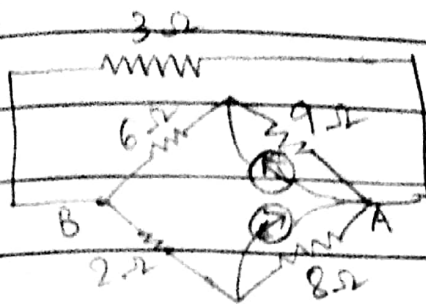


$$V_{ab} = -2 \times 1 = -2V$$

$$V_{ab} = 2 \times 1 = 2V$$

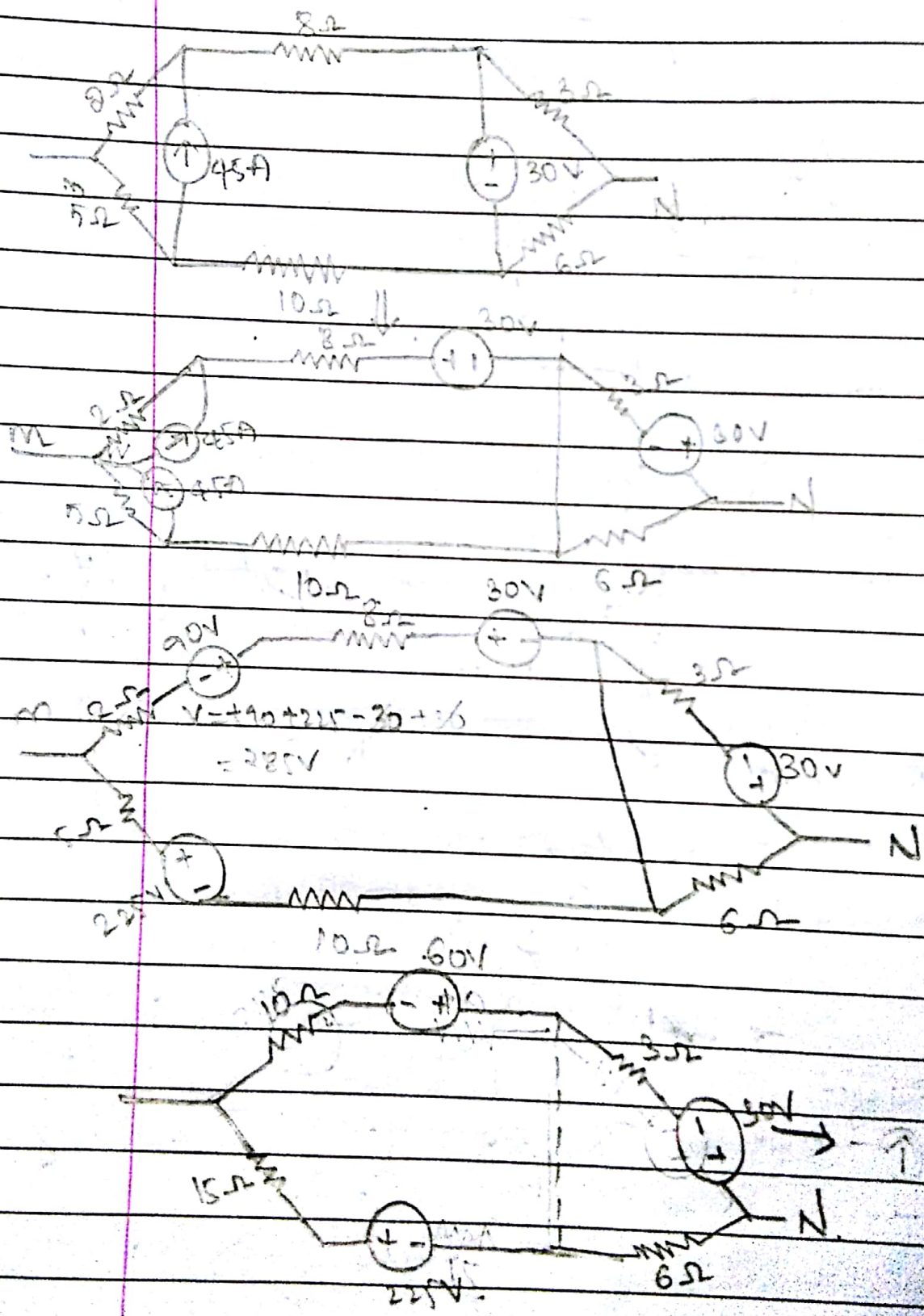⑦ Convert the follⁿ ckt into single voltage source by applying source shifting and source transformation



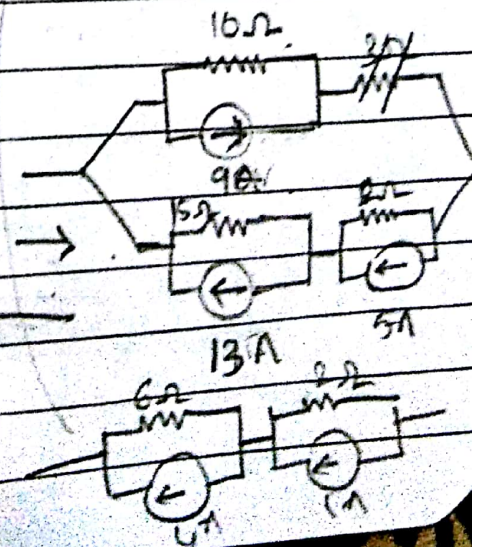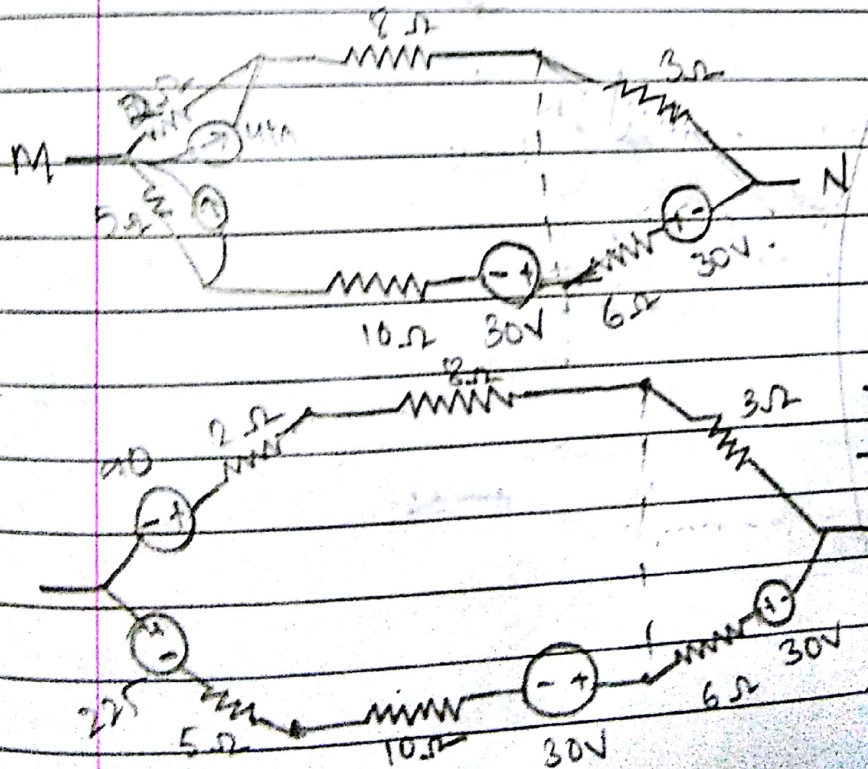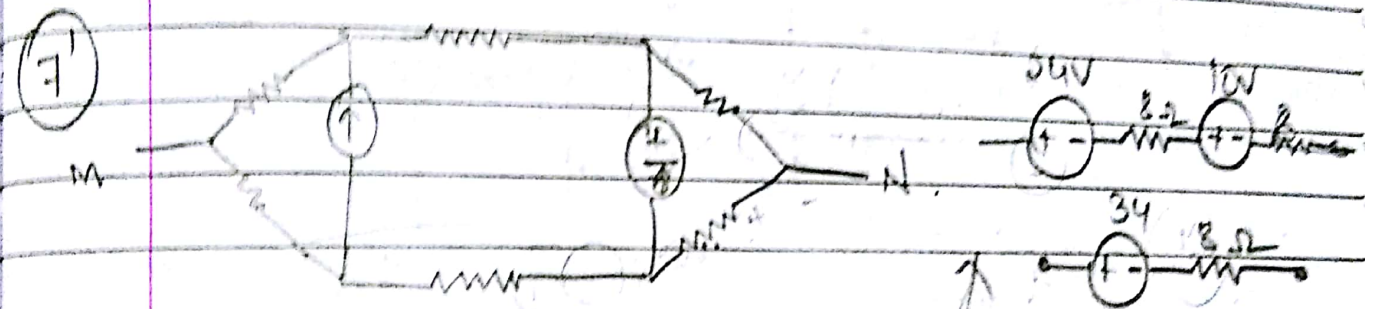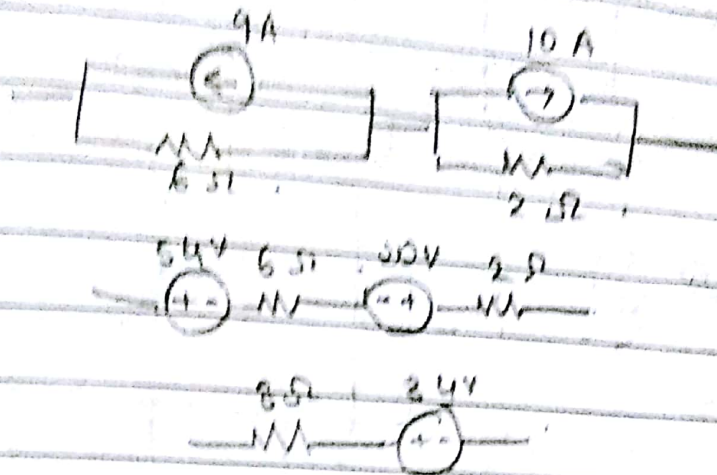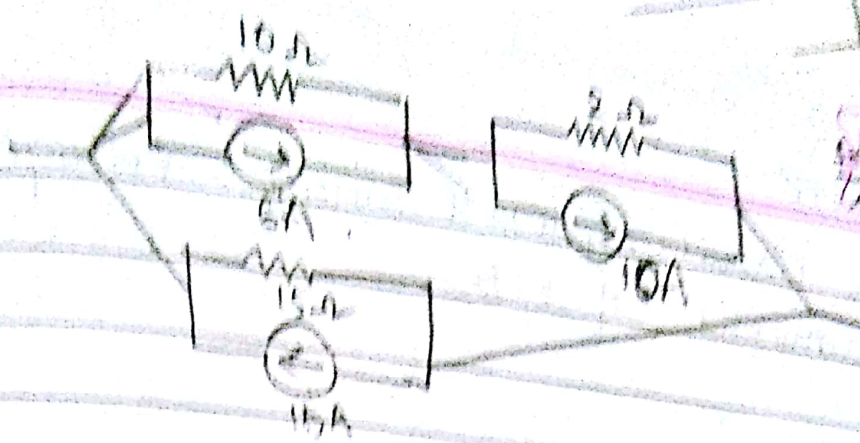





Redesign the Steps and Potentials:

Review Questions:

1. Reduce the circuit shown to single voltage source b/w terminals A & B.

PAGE NO.:




DATE: / /

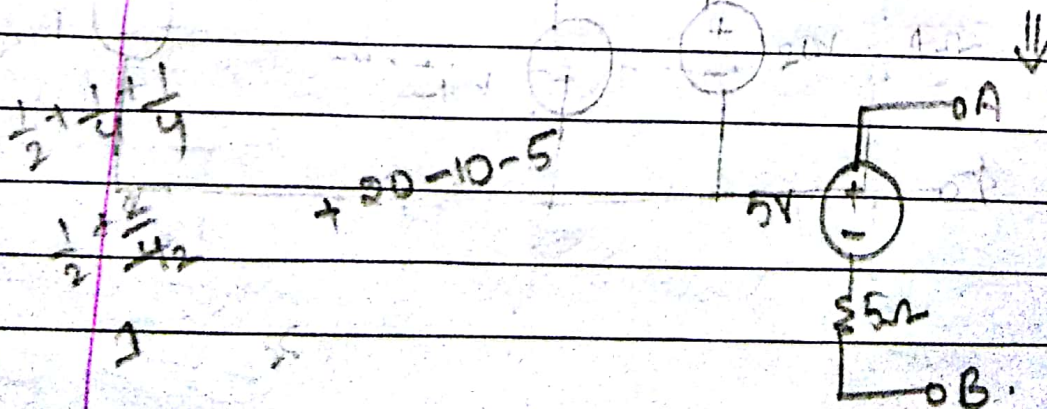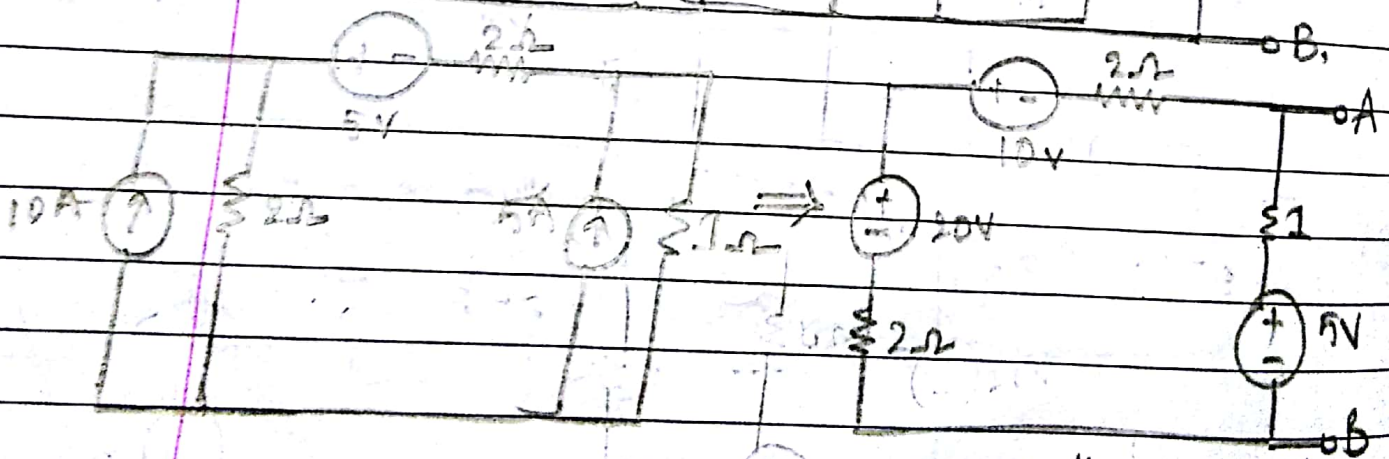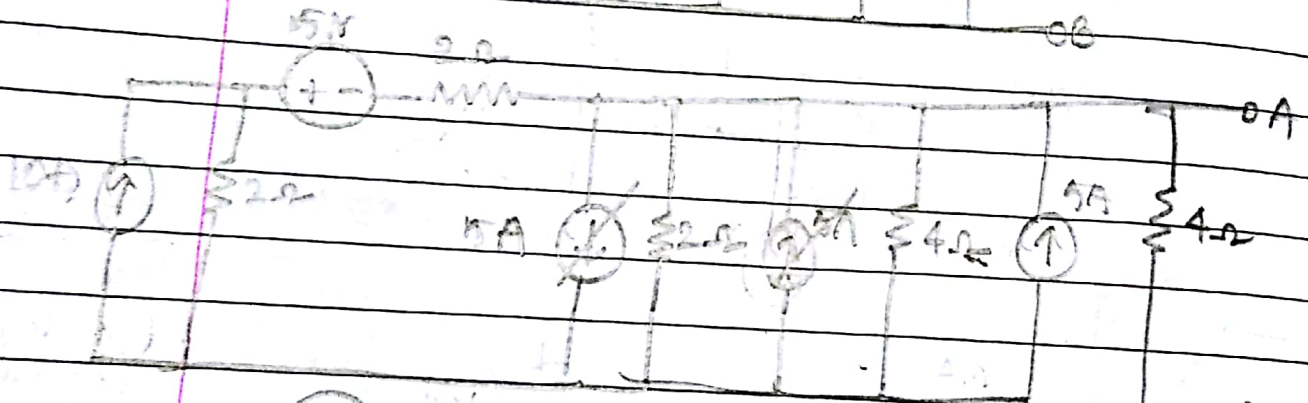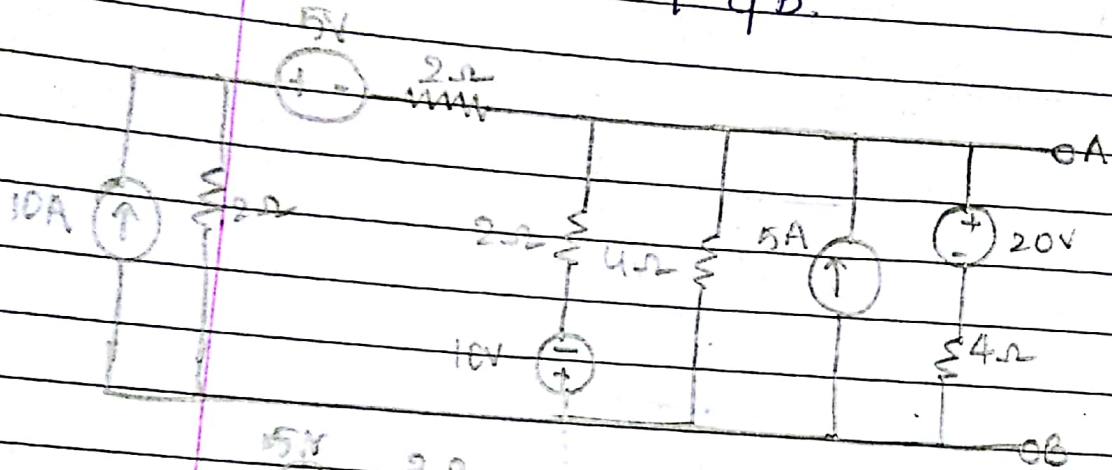

$$\frac{1}{2} + \frac{1}{4} + \frac{1}{4}$$


$$\frac{1}{2} + \frac{2}{4}$$

$$+ 20 - 10 - 5$$

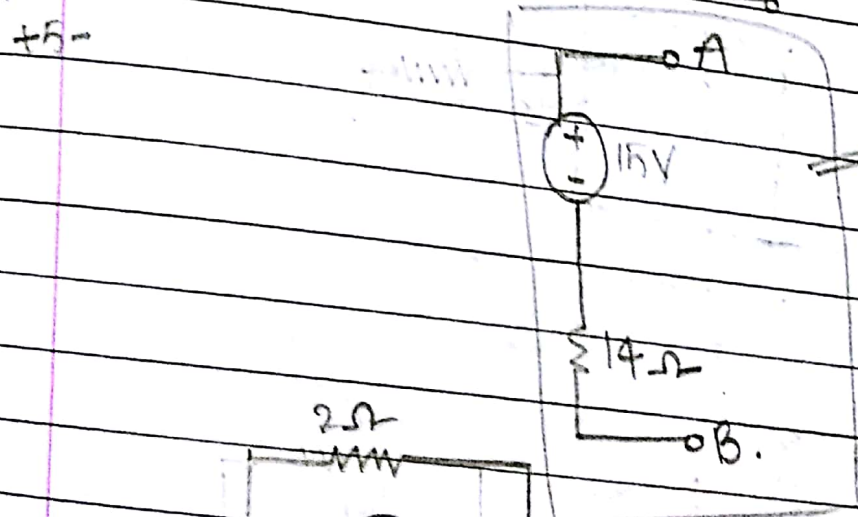
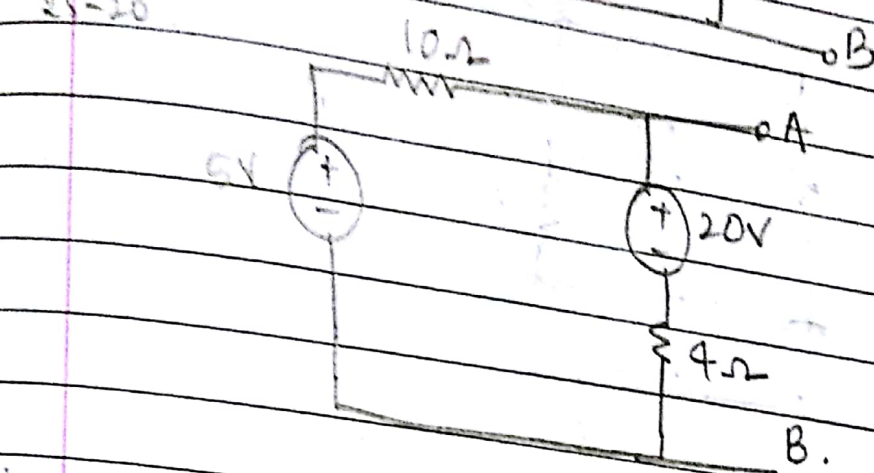
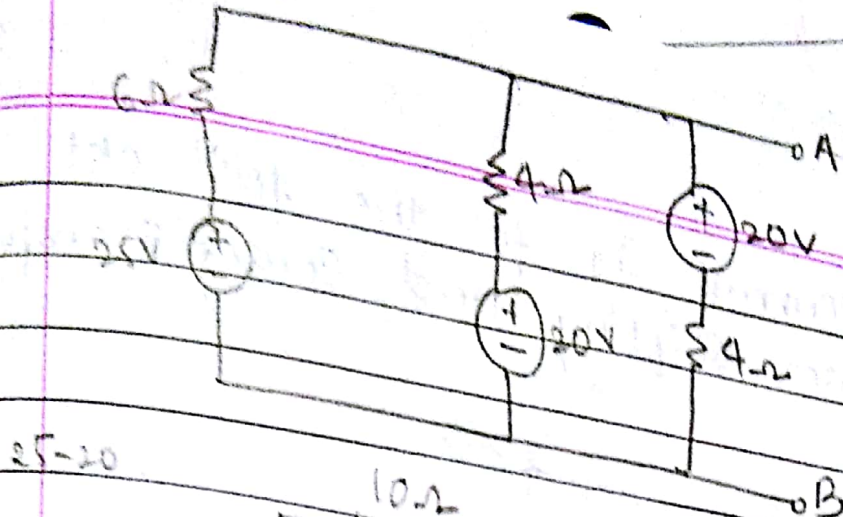


Ans.

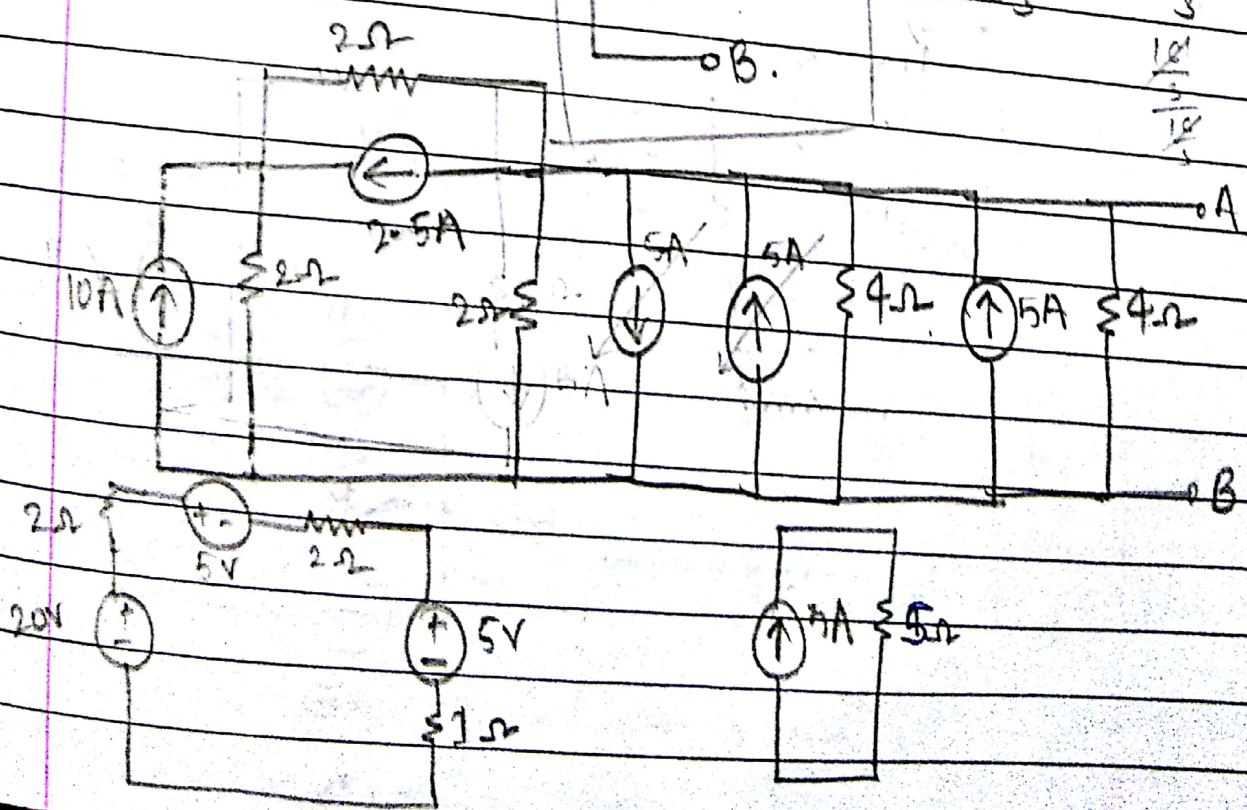
$$\frac{4 \times 4}{8} = \frac{4}{3} \quad \frac{\frac{4}{3} + 4}{\frac{16}{3}} = \frac{16}{5}$$




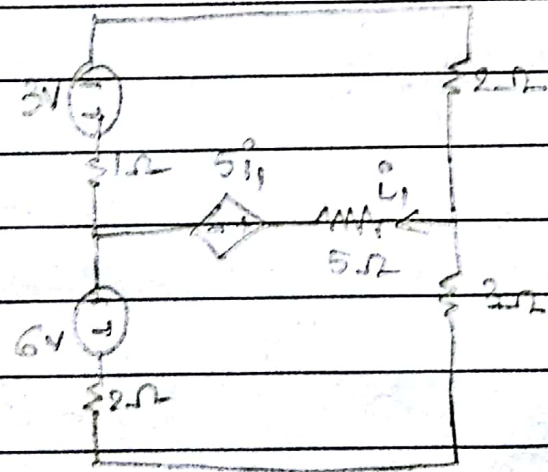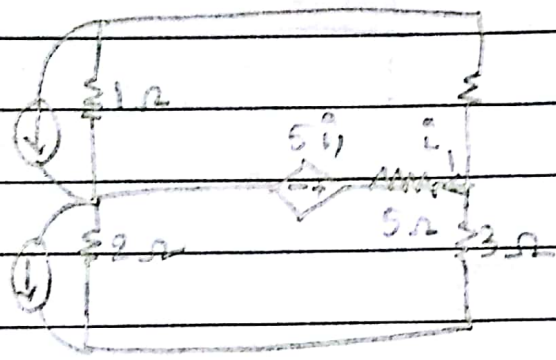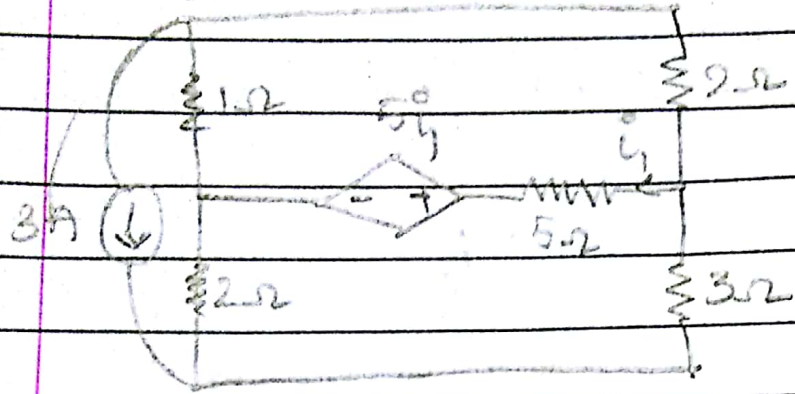⑧. Determine current I_1 for the follⁿ ckt using source shifting and source transformation.


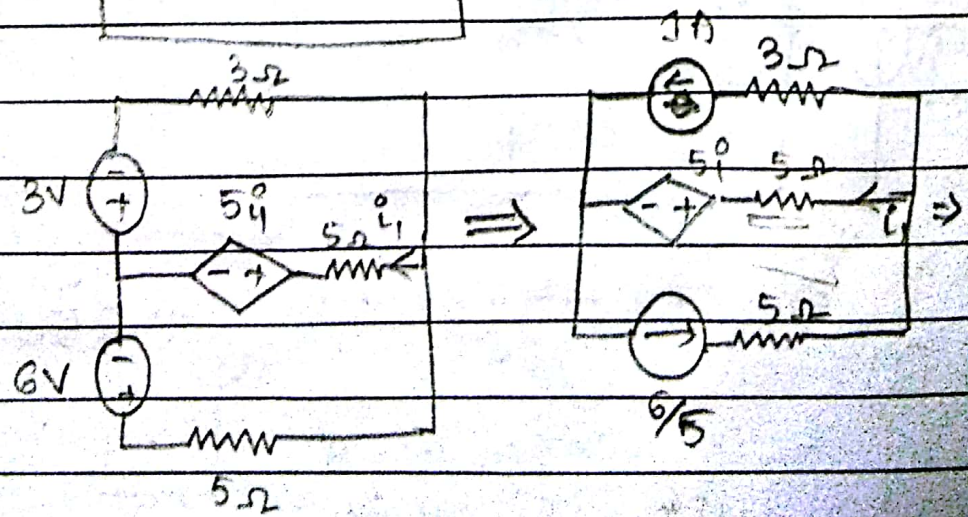
$$\frac{1}{-1 + \frac{6}{5}} = \frac{1}{5}$$



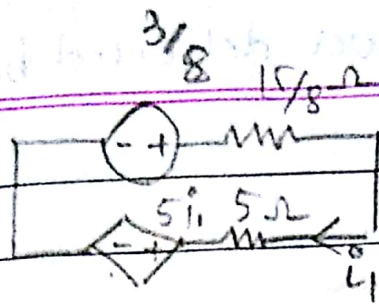

$$-5i_1 - 5i_1 + \frac{3}{8} - \frac{15}{8}i_1 = 0$$


$$i_1(-10 - \frac{15}{8}) = -\frac{3}{8}$$

$$i_1 \frac{95}{8} = \frac{3}{8}$$


$$i_1 = \frac{3}{95}$$

$$i_1 = 31.578 \text{ mA}$$

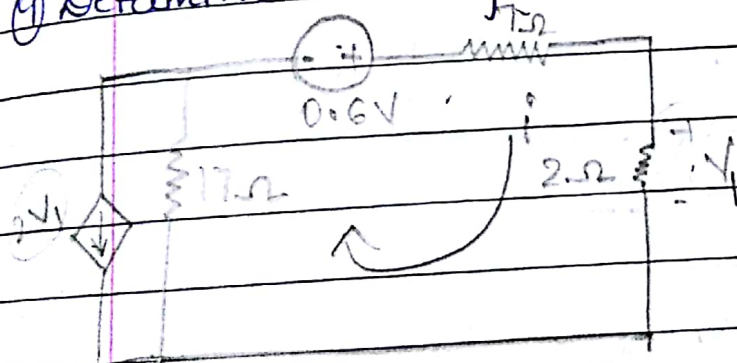Q Determine Voltage V_1 using Source Transformation.



$$V = 2i_1$$

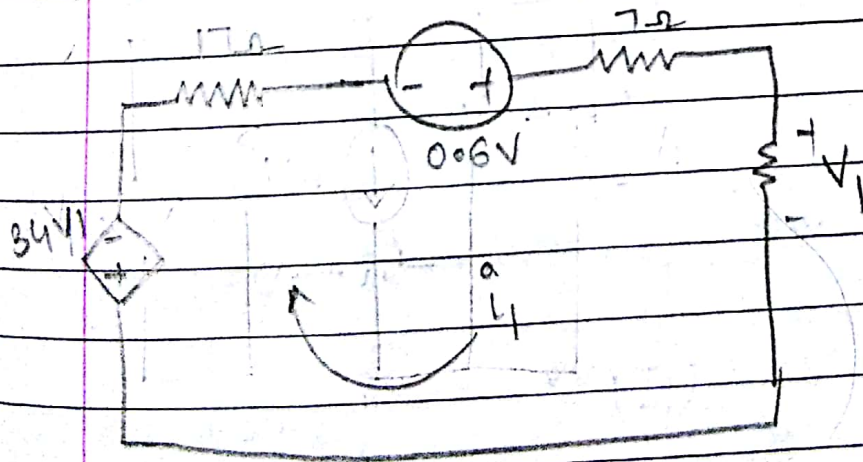

$$V_1 = i_1 R$$

$$= 2i_1$$

$$V_1 = 2 \times 12.76 \text{ mV}$$

$$-34V_1 - 17i_1 + 0.6V_1 - 7i_1 - V_1 = 0 \quad i_1 = 6.382$$

$$-38V_1 - 17i_1 + \frac{0.6}{2}V_1 - 7i_1 - 2i_1 = 0$$





Om Sai:

... ..

PAGE NO.:

Find current i and also power delivered by $50V$

(10).

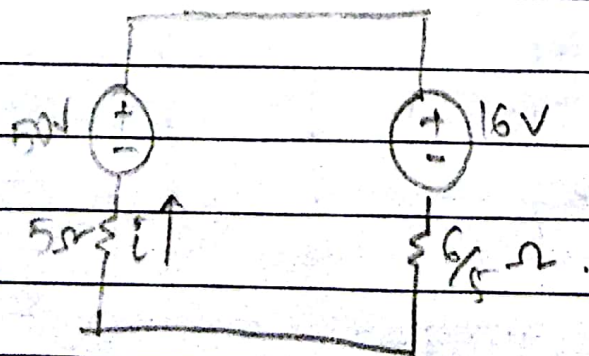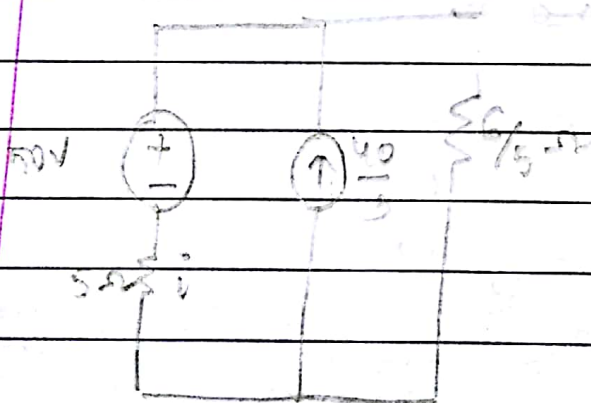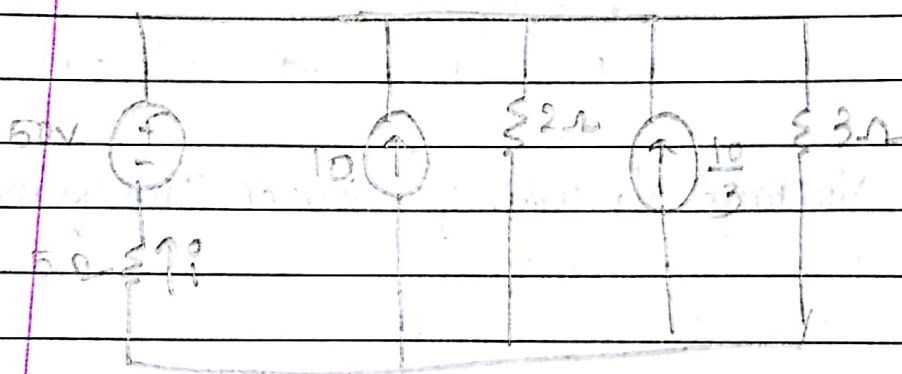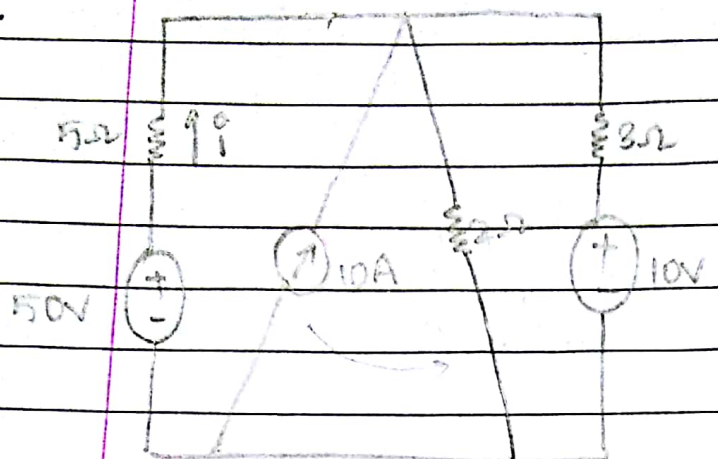

$$-5i + 50 - 16 - \frac{6}{5}i = 0$$


$$34 = \left(5 + \frac{6}{5}\right)i$$

$$34 = \frac{31}{5}i$$

$$P = VI = 50 \times 5.48 = 274.19W$$

MESH ANALYSIS

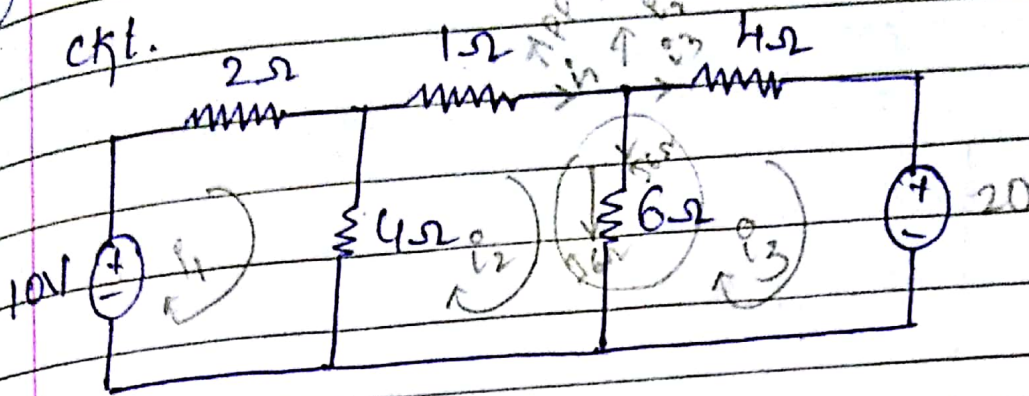① Determine current through 6Ω resistor in folⁿ ckt.



$$10 - 2i_1 - 4(i_1 - i_2) = 0$$

$$10 - 2i_1 - 4i_1 + 4i_2 = 0$$

$$10 = 6i_1 - 4i_2$$

$$0 = 10 - 6i_1 + 4i_2 \rightarrow \textcircled{1}$$

$$-4(i_2 - i_1) - i_2 - 6(i_2 - i_3) = 0$$

$$-4i_2 + 4i_1 - i_2 - 6i_2 + 6i_3 = 0$$

$$-11i_2 + 4i_1 + 6i_3 = 0 \rightarrow \textcircled{2}$$

$$-6(i_3 - i_2) - 4i_3 = 20$$

$$-6i_3 + 6i_2 - 4i_3 = 20$$

$$6i_2 - 10i_3 = 20 \rightarrow \textcircled{3}$$

6V

$$\text{Ans: } \begin{bmatrix} 6 & -4 & 0 \\ 4 & -11 & 6 \\ 0 & 6 & -10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 20 \end{bmatrix}$$


$$x = 65/11$$

$$y = -80/11 \quad z = -190/11$$

$$i_1 = 0.9152 \quad i_2 = -1.126 \quad i_3 = -2.676$$

$$i = -1.126 \text{ A} \quad -2.676$$

Q) Determine all loop currents in ckt.

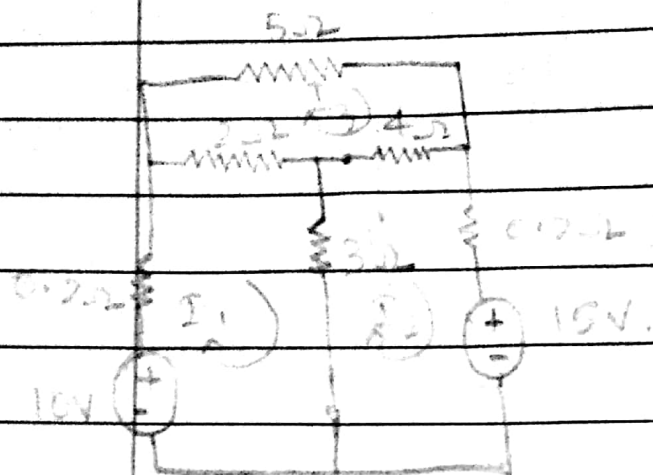

$$-3(I_1 - I_2) - 4(I_2 - I_3) - 0.2I_2 = 0$$

$$-3I_1 + 3I_2 - 4I_2 + 4I_3 - 0.2I_2 = 0$$

$$-3I_1 - I_2 + 4I_3 = 0$$

$$-3(I_2 - I_1) - 4(I_2 - I_3) - 0.2I_2 = 15$$

$$-3I_2 + 3I_1 - 4I_2 + 4I_3 - 0.2I_2 = 15$$

$$3I_1 - 7.2I_2 + 4I_3 = 15$$

$$-3(I_3 - I_1) - 5I_3 - 4(I_3 - I_2) = 0$$

$$-3I_3 + 3I_1 - 5I_3 - 4I_3 + 4I_2 = 0$$

$$3I_1 + 4I_2 - 12I_3 = 0$$

$$\begin{bmatrix} -5.2 & 3 & 2 \\ 3 & -7.2 & 4 \\ 3 & 4 & -11 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -10 \\ 15 \\ 0 \end{bmatrix}$$


$$I_1 = 0.11A, I_2 = 0.11A, I_3 = 0.11A$$

$$I_1 = \begin{vmatrix} -10 & 3 & 2 \\ 15 & 7.2 & 4 \\ 0 & 4 & 11 \end{vmatrix}$$


$$I_2 = \begin{vmatrix} 5.2 & 3 & 2 \\ 3 & -7.2 & 4 \\ 2 & 4 & -11 \end{vmatrix}$$

$$I_1 = 0.11 \text{ A}$$

Ckt Analysis using SuperMesh:

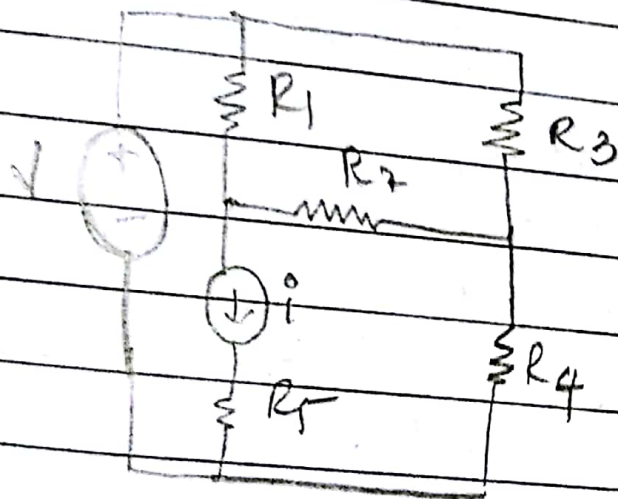

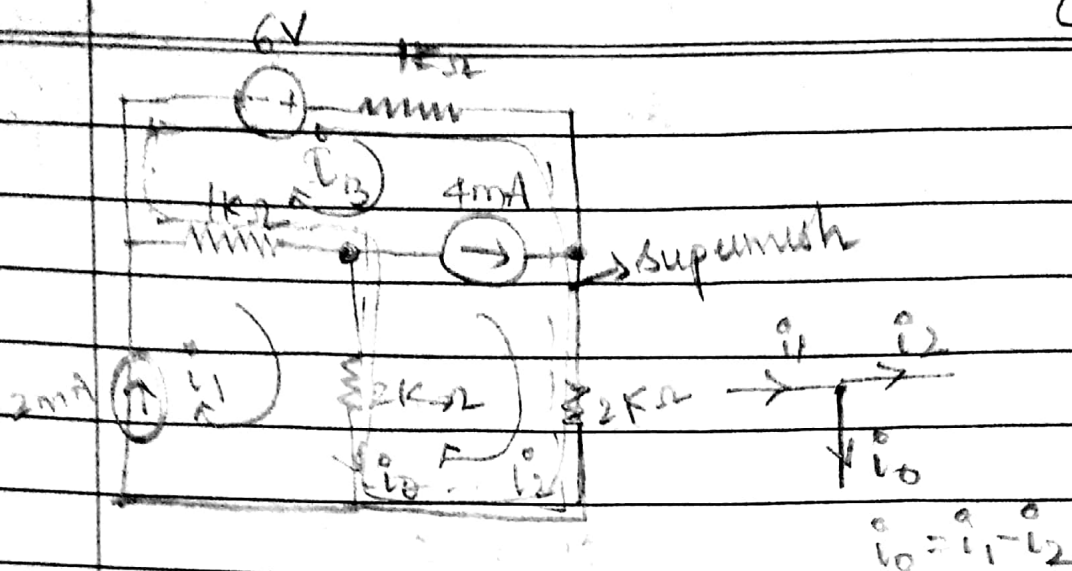
* Find i_0 in the follⁿ ckt using Supermesh.



Constraint Eqⁿ.


$$i_0 = i_1 - i_2$$

$$i_1 = 2\text{mA}$$

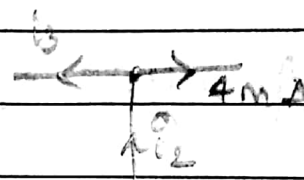

$$i_2 - i_3 = 4\text{mA}$$

Applying KVL to Supermesh.

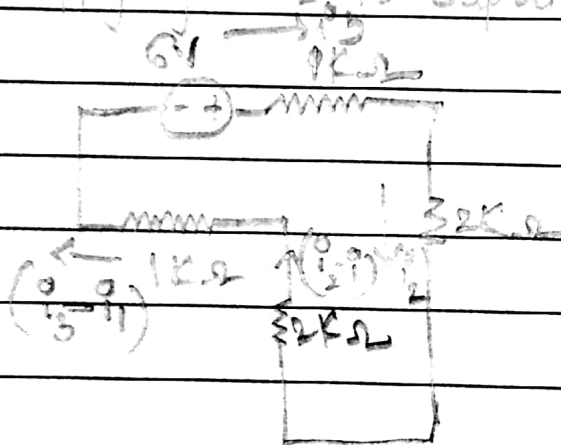

$$6 - 1i_3 - 2i_2 - 2(i_2 - i_1) - (i_3 - i_1) = 0$$

$$6 - i_3 - 2i_2 - 2i_2 + 2i_1 - i_3 + i_1 = 0$$

$$6 - 2i_3 - 4i_2 + 2i_1 = 0$$

$$6 = 3i_1 + 4i_2 + 2i_3$$

$$6 = -3i_1 + 4i_2 + 2i_3$$

$$6 = -6 + 4i_2 + 2i_3$$

$$12 = 4i_2 + 2i_3$$

$$3i_2 = 8 \text{ mA}$$

$$4i_2 + 2i_3 = 12 \text{ mA}$$

$$3i_2 = 10$$

$$i_2 = 3.3 \text{ mA}$$



$$3.3 - i_3 = 4 \text{ mA}$$

$$i_3 = -0.667 \text{ mA}$$

$$i_0 = i_1 - i_2$$

$$i_0 = -1.03 \text{ mA}$$

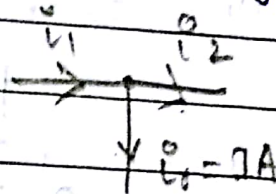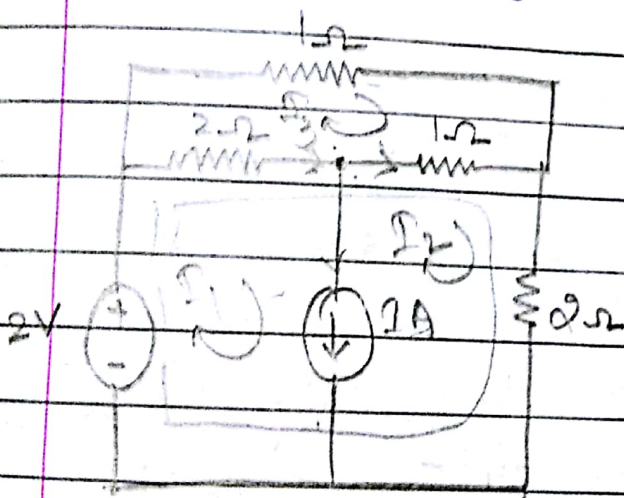* Determine P_1, P_2, P_3 in the follⁿ using supernode.



$$-i_0 - i_2 = i_1$$

$$+1 = i_1 + i_2$$

$$i_1 - i_2 = 1$$

$$2 - 2(i_1 - i_3) + 1(i_3 - i_2) - 2i_2 = 0$$

$$2 - 2i_1 + 2i_3 + i_2 + i_3 - 2i_2 = 0$$

$$2 - 2i_1 + 3i_3 - 3i_2 = 0$$

$$2 = 2i_1 + 3i_2 - 3i_3$$

$$-i_3 - 1(i_3 - i_2) - 2(i_3 - i_1) = 0$$

$$-i_3 - i_3 + i_2 - 2i_3 + 2i_1 = 0$$

$$2i_1 + i_2 - 4i_3 = 0$$

$$2I_1 + I_2 = 4I_3$$

$$2I_1 + 3I_2 - \frac{3}{4}(2I_1 + I_2) = 2$$

$$8I_1 + 12I_2 - 6I_1 - 3I_2 = 8$$

$$2I_1 + 9I_2 = 8$$

$$9I_1 - 9I_2 = 9$$

$$11I_1 = 17$$

$$I_1 = \frac{17}{11} = 1.5$$

$$I_1 - I_2 = 1$$

$$\frac{17}{11} - 1 = I_2$$

$$0.54 = \frac{6}{11} = I_2$$

$$\frac{2 \times 17}{11} + \frac{6}{11} = 4I_3$$

$$\frac{34 + 6}{11} = 4I_3$$

$$\frac{40}{11} = 4I_3$$


$$I_3 = \frac{10}{11}$$

$$= 0.90$$

④ Determine all 3 loop current in ckt

PAGE NO.:

DATE: / /

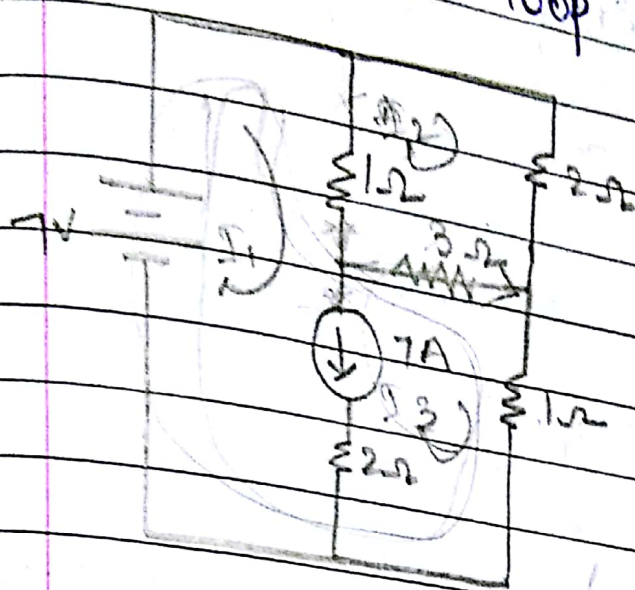


$$I_1 - I_3 = 7$$

$$7 - 1(I_1 - I_1) - 3(I_2 - I_1) - 1(I_3) = 0$$

$$7 - I_2 + I_1 - 3I_2 + 3I_1 - I_3 = 0$$

$$7 + 2I_1 - 4I_2 - I_3 = 0$$

$$7 = -2I_1 + 4I_2 + I_3$$

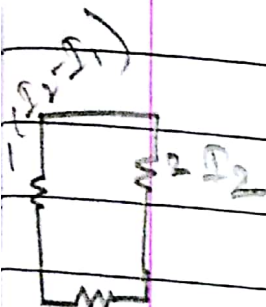

$$3(I_2 - I_3)$$

$$-1(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) = 0$$

$$-I_2 + I_1 - 2I_2 - 3I_2 + 3I_3 = 0$$

$$I_1 - 6I_2 + 3I_3 = 0$$

6

$$I_1 + 3I_3 = 6I_2$$

$$7 = -I_1 - 2(-I_1 + 3I_3) + 14I_2$$

$$42 = -6I_1 - 2I_1 + 6I_3 + 14I_2$$

$$42 = -8I_1 + 6I_3 + 14I_2$$


$$58 = 8I_1 - 8I_3$$

$$I_3 = 2.33A$$

$$98 = 2I_3$$


$$I_3 = 2.33A$$

⑤ Determine current i_o using supermesh.

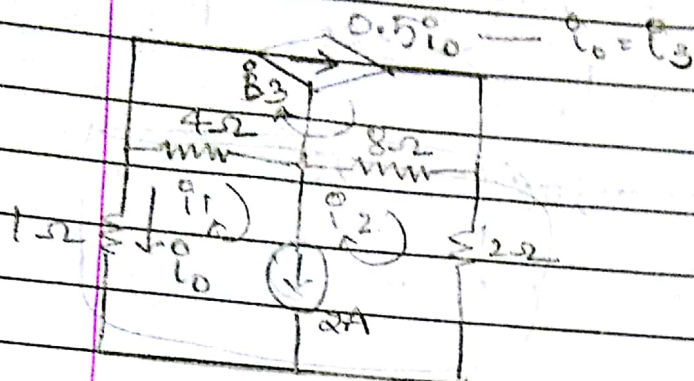

Applying KVL to Supermesh
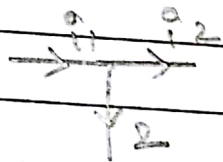
$$\begin{aligned} -i_1 - 4(i_1 - i_3) - 8(i_2 - i_3) - 2i_2 &= 0 \\ -i_1 - 4i_1 + 4i_3 - 8i_2 + 8i_3 - 2i_2 &= 0 \\ -5i_1 + 12i_3 - 10i_2 &= 0 \end{aligned}$$



$$i_1 - 2 - i_2 = 0$$

$$i_1 - i_2 = 2$$

and also $i_o = -i_1$

$$0.5i_o = -0.5i_1$$

$$\begin{aligned} -4(i_1 - i_3) - 0.5i_o - 8(i_2 - i_3) &= 0 \\ -4i_1 + 4i_3 - 0.5i_1 - 8i_2 + 8i_3 &= 0 \end{aligned}$$

$$3.5i_1 - 12i_3 + 8i_2 = 0$$

$$3.5i_1 + 12 \times 0.5i_1 + 8i_2 = 0$$

$$9.5i_1 + 8i_2 = 0$$

don't take i_o because flowing in loop 1

$$8i_1 - 8i_2 = 16$$

$$9.5i_1 + 8i_2 = 0$$

$$17.5i_1 = 16$$

$$i_1 = 16$$

$$17.5$$

$$i_1 = 0.9142$$

$$i_0 = -i_1 = -0.9142 \text{ A}$$



$$9.5 \times 0.9142 + 8i_2 = 0$$

$$i_2 = -1.085 \text{ A}$$

$$-5 \times 0.9142 + 12i_3 + 10 \times 1.085 = 0$$

$$i_3 = -0.4571 \text{ A}$$

NODAL ANALYSIS: Node Voltage Source.

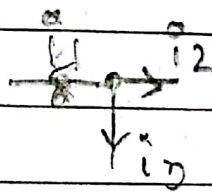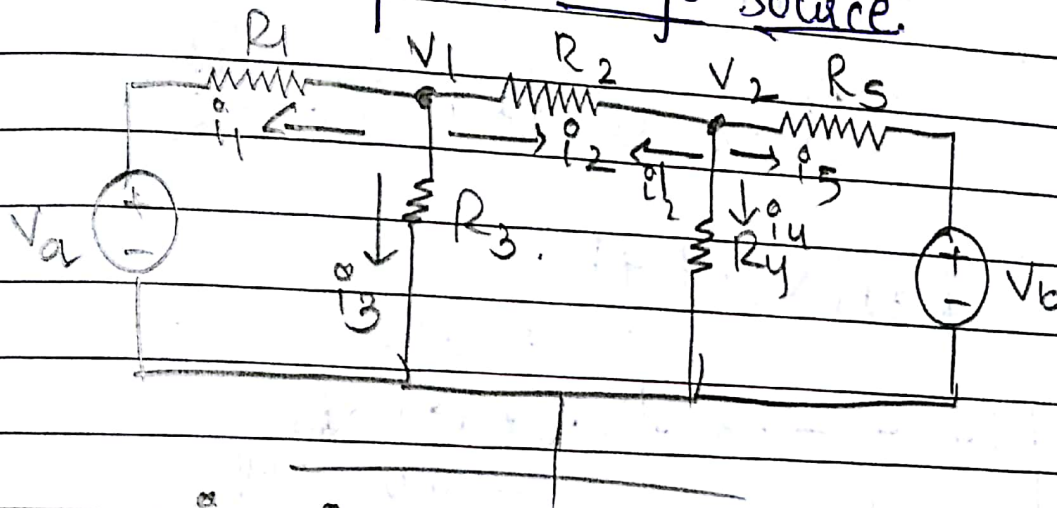

$$i_1 + i_2 + i_3 = 0$$

At node V_1 :

$$\frac{V_1 - V_a}{R_1} + \frac{V_1}{R_3} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1 - V_a}{R_1} + \frac{V_1}{R_3} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_1}{R_1} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{V_2}{R_2} = \frac{V_a}{R_1}$$

At node V_2

$$-i_2 - i_4 - i_5 = 0$$

$$i_2 + i_4 + i_5 = 0$$

$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - V_b}{R_5} + \frac{V_2}{R_4} = 0$$


$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - V_b}{R_5} + \frac{V_2}{R_4} = 0$$


$$V_2 \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_1}{R_2} = \frac{V_b}{R_5}$$

$$[G][V] = [I]$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{V_{a1}}{R_1} \\ \frac{V_{b2}}{R_5} \end{bmatrix}$$

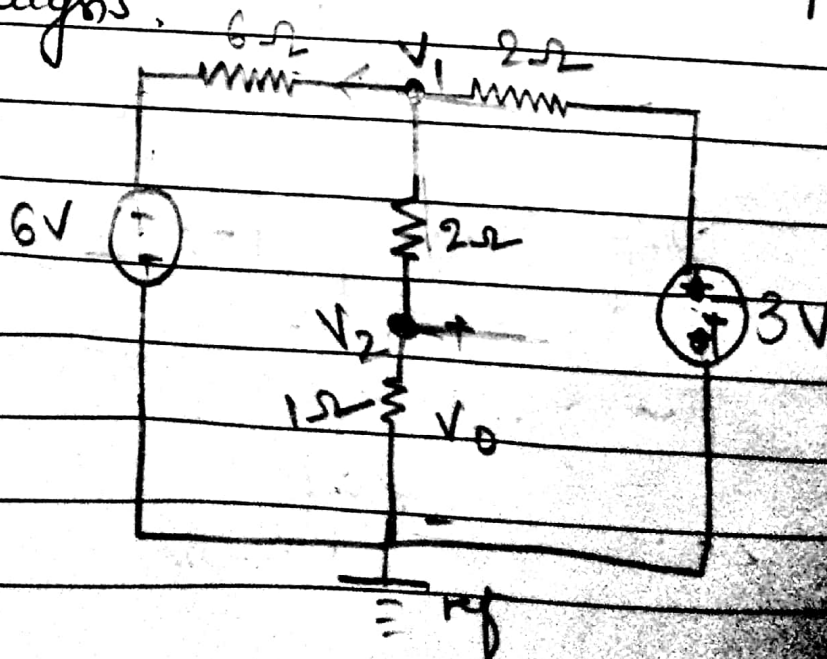Ex: ①. Determine voltage V_0 in follⁿ ckt using Nodal Analysis.



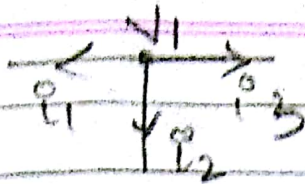

$$i_1 + i_2 + i_3 = 0$$

$$\frac{V_1 + 6}{6} + \frac{(V_1 - V_2)}{2} + \frac{V_1 + 3}{2} = 0$$

$$\frac{V_1 + 1}{6} + \frac{V_1 - V_2}{2} + \frac{V_1 + 3}{2} = 0$$

$$V_1 \left(\frac{1}{6} + \frac{1}{2} + \frac{1}{2} \right) - \frac{V_2}{2} = +1 + 3$$

$$V_1 \frac{7}{6} - \frac{V_2}{2} = \frac{4}{2}$$

$$\left(\frac{V_2 - V_1}{2} \right) + \frac{V_2}{1} = 0$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} = 0$$

$$V_2 \left(\frac{3}{2} \right) - \frac{V_1}{2} = 0$$


$$-\frac{V_1}{2} + V_2 \left(\frac{3}{2} \right) = 0$$

$$\begin{bmatrix} \frac{7}{6} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{3}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -\frac{4}{2} \\ 0 \end{bmatrix}$$

$$V_1 = -0.5V$$

$$V_2 = 0.1567V = 0.833V$$

(51)

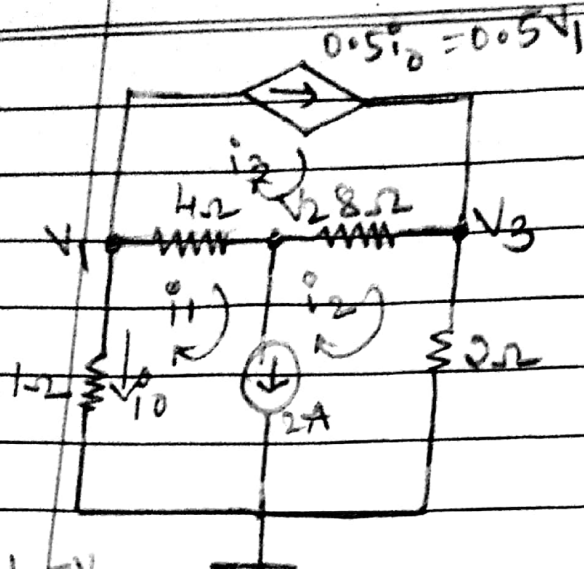

$$i_0 = \frac{V_1}{1} = V_1$$

$$\frac{V_1}{4} + 0.5V_1 + \frac{V_1}{1} = 0$$

$$V(0.25 + 0.5 + 1) = \frac{N_2}{4}$$

$$V(1.75) = \frac{N_2}{4}$$

$$\frac{V_2 - V_1}{4} + 2 + \frac{V_2 - V_3}{8} = 0$$

$$\frac{V_2 - V_1}{4} + 2 + \frac{V_2 - V_3}{8} = 0$$

$$\frac{V_1}{4} + \frac{V_3}{8} - 0.375V_2 = -2$$

$$\frac{N_1}{4} - 0.375V_2 + \frac{V_3}{8} = 2$$

$$\frac{V_3}{2} + \frac{V_3 - V_2}{8} - 0.5V_1 = 0$$

$$\frac{V_3}{2} + \frac{V_3 - V_2}{8} - 0.5V_1 = 0$$

$$0.625V_3 - \frac{V_2}{8} - 0.5V_1 = 0$$


$$V_1 = -0.952V$$

$$V_2 = -6.06V$$

$$V_3 = -2.09V$$

$$\begin{bmatrix} 1.75 & -1/4 & 0 \\ 1/4 & -0.375 & 1/8 \\ -0.5 & 1/8 & 0.625 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ 0 \end{bmatrix}$$

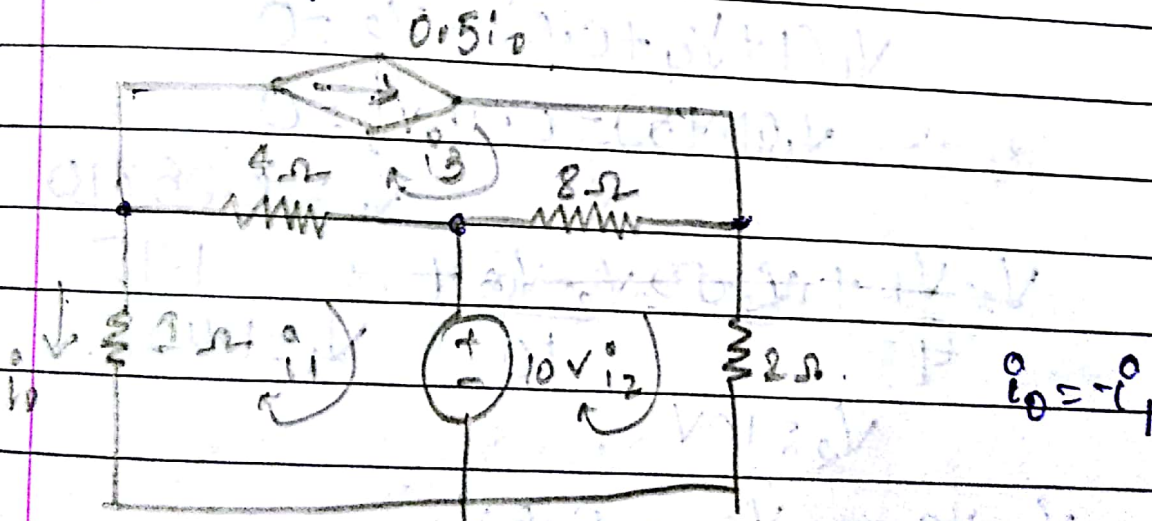8) Determine Current I_0 using Mesh and Nodal Analysis for follⁿ ckt



loop 1 $-I_1 - 4(I_1 - I_3) = 10$

$$-I_1 - 4I_1 + 4I_3 = 10$$

$$-5I_1 + 4I_3 = 10$$

$$10 = +10I_2 - 8I_3$$

loop 3

$$-4(I_3 - I_1) + 0.5I_0 - 8(I_3 - I_2) = 0$$

$$(I_3 - I_2) = 0$$

loop 2 $10 - 8(I_2 - I_3) - 2I_2 = 0$

$$10 - 8I_2 + 8I_3 - 2I_2 = 0$$

$$-4i_3 + 4i_1 + 0.5i_0 - 8i_3 + 8i_2 = 0$$

$$-4i_3 + 4i_1 - 0.5i_1 - 8i_3 + 8i_2 = 0$$

$$-12i_3 - 4i_5i_1 + 8i_2 = 0$$

$$+5i_0 + 4(0.5i_0) = 10$$

$$5i_0 + 2i_0 = 10$$

$$i_0 = \frac{10}{7} \text{ A}$$

Nodal Analysis:

$$i_0 = \frac{V_1}{1}$$

$$\frac{V_1}{1} + \frac{V_1 - V_2}{4} = -0.5i_0$$

$$= -0.5V_1$$

$$V_1 + \frac{V_1 - V_2}{4} + 0.5V_1 = 0$$

$$V_1(1 + 0.25 + 0.5) - \frac{V_2}{4} = 0$$

$$V_1(1.75) - 0.25V_2 = 0$$

$$V_1 = 0.25 \times 10$$

$$\frac{V_2 - V_1}{4} + \frac{V_2 - V_3}{10} + \frac{V_2 - V_3}{10} = 0$$

$$1.75$$

$$V_1 = 1.428$$

$$V_2 = 10 \text{ V}$$

$$\frac{V_3 - V_2}{8} + \frac{V_3}{2} = 0.5V_1$$

$$\frac{V_3 - V_2}{8} + \frac{V_3}{2} - 0.5V_1 = 0$$

$$V_3\left(\frac{1}{8} + \frac{1}{2}\right) - \frac{V_2}{8} - 0.5V_1 = 0$$

$$V_3(0.625) - \frac{10}{8} - 0.5V_1 = 0$$

$$V_3(0.625) - 1.25 - 0.5V_1 = 0$$

$$V_3(0.625) = 1.25 - 1.428 \times 0.5 = 0$$



$$V_3 = 1.964$$

$$V_3 = \frac{0.625}{8.1424}$$

PAGE NO.:

DATE: / /

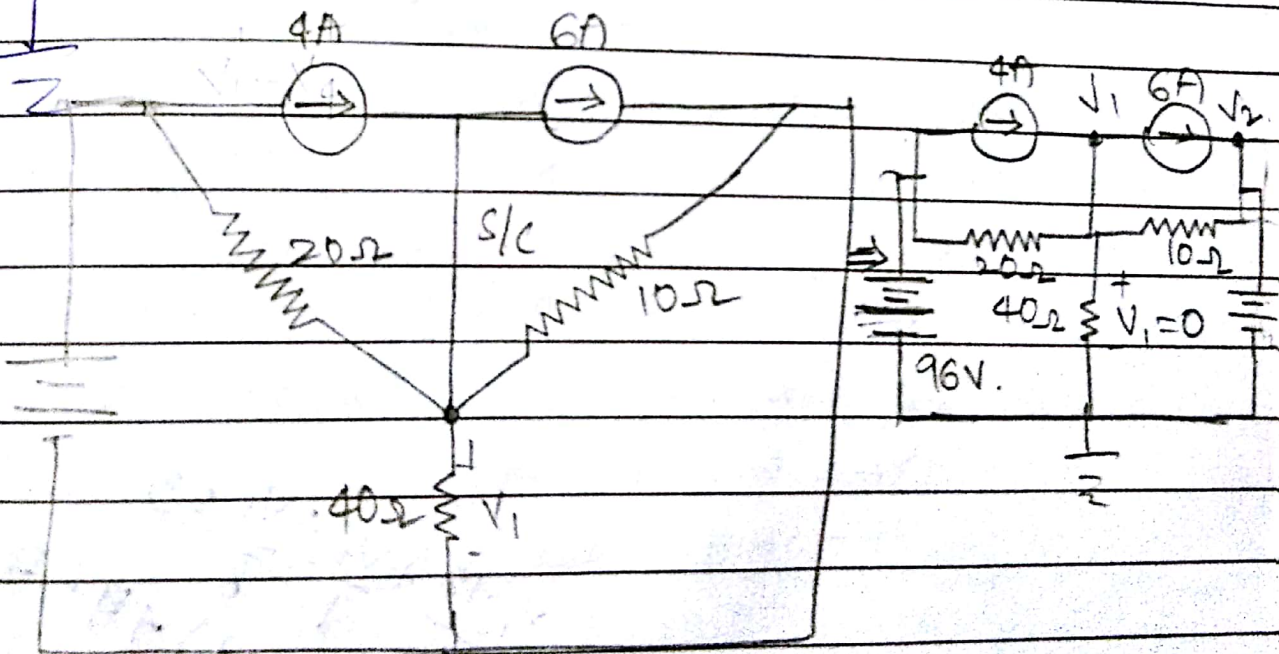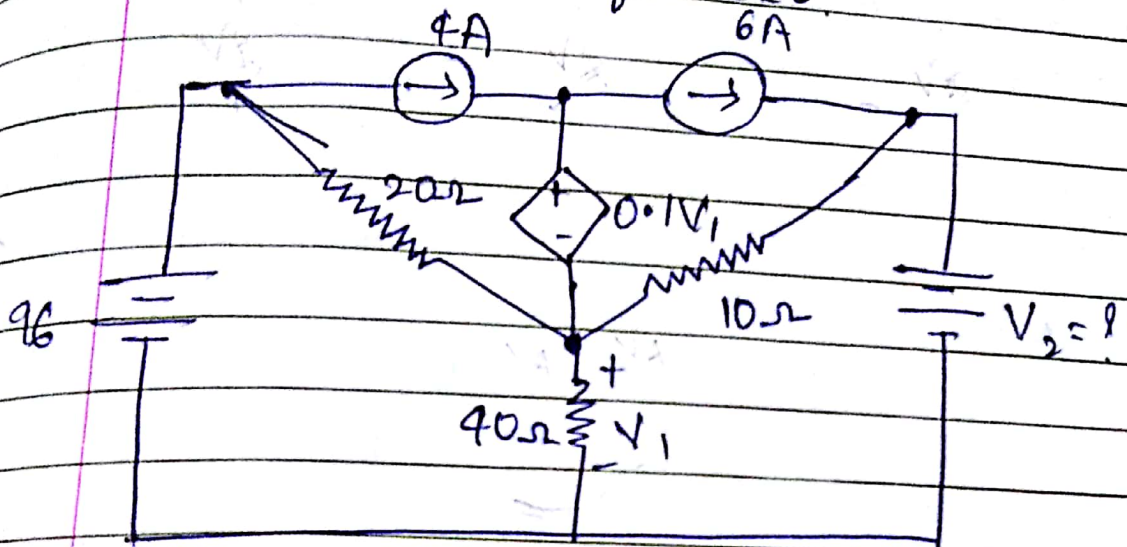Use Nodal Analysis to determine value of V_2 that will result in $V_1 = 0$ in given ckt.




$$\frac{V_1 - 96}{20} + \frac{V_1 - V_2}{10} + \frac{V_1}{40} = -6 + 4$$

$$-\frac{96}{20} - \frac{V_2}{10} = -2$$

$$\frac{V_2}{10} = -\frac{96}{20} + 2 \Rightarrow V_2 = -28V$$

$$\frac{96}{20} + \frac{V_2}{10} = -2 \Rightarrow \frac{V_2}{10} = -2 - \frac{96}{20} \Rightarrow V_2 = -28V$$

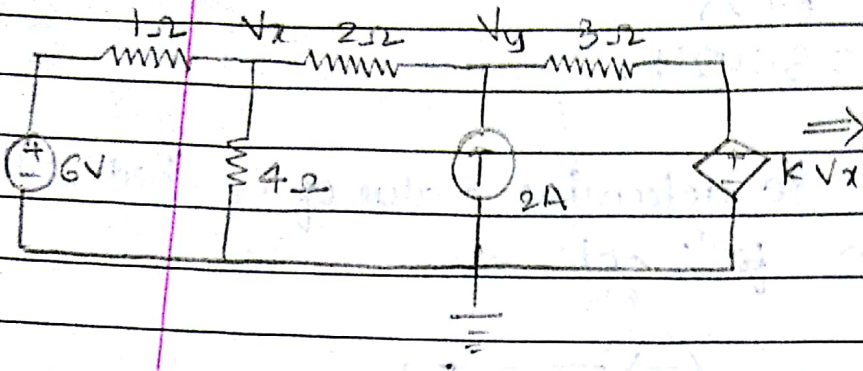using Nodal Analysis Determine value of K which we cause $V_y = 0$.



$$\frac{V_x - 6}{1} + \frac{V_x}{4} + \frac{V_x - V_y}{2} = 0$$

$$\frac{V_y}{3} \quad V_x - 6 + \frac{V_x}{4} + \frac{V_x - V_y}{2} = 0$$

$$V_x \left(1 + \frac{1}{2} + \frac{1}{4}\right) = 6$$

$$V_x = 3.42 \text{ V}$$

$$+2 = \frac{V_y - K V_x}{3} + \frac{V_y}{2} - \frac{V_x}{2}$$

$$2 = \frac{-K(3.42) - 3.42}{3} - \frac{3.42}{2}$$

$$K = -3.25 \text{ V}$$

$$3 \left(2 + \frac{1}{3} + \frac{1}{4}\right) \quad \frac{V_1 - 12}{3} + \frac{V_1}{1} + \frac{V_1}{8} = 3$$


$$\frac{V_1}{8} \left(\frac{1}{3} + 1 + \frac{1}{8}\right) + 19 = 7$$

Supernode Analysis: (Can't Ideal Voltage Source)

When network has an ideal voltage source as one of its branches then the current through this voltage source cannot be determined and it should be noted that this V.S is present b/w 2 nodes hence these two nodes can be considered as one node which is called as super node. using this supernode no. of KCL eq^s can be reduced by 2.

[P.S note that this ideal source must be b/w non-ref. node. Then only supernode can be considered.]

Ex: (1) Determine V_o

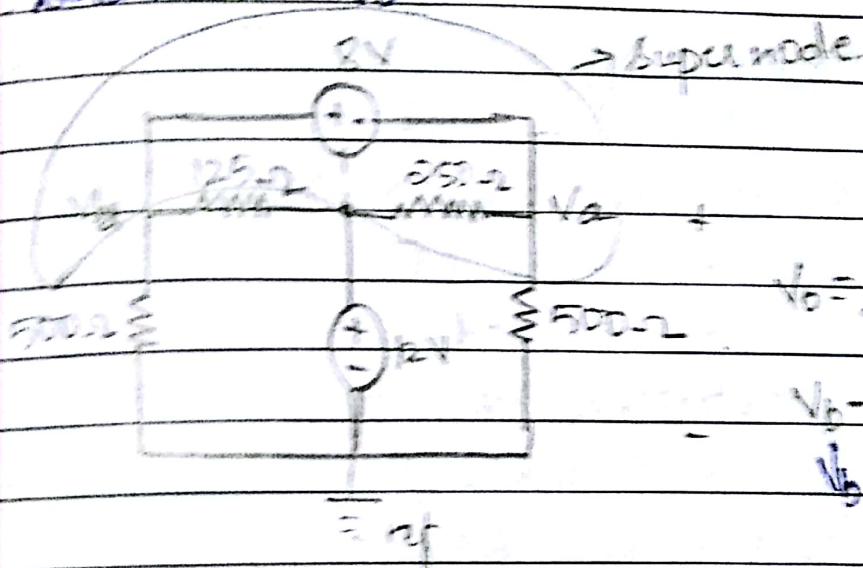

$$\begin{aligned} V_1 - 0 + \frac{V_1}{8} &= 3 \\ \frac{V_1}{3} + \frac{V_1}{8} &= 3 \\ V_1 - 4 + \frac{V_1}{8} &= 3 \end{aligned}$$

$$V_o = 0$$

$$V_1 - V_2 = 8$$

$$V_1 = 8 + V_2$$

Applying KCL at supernode.

$$\frac{V_1}{500} + \frac{V_1 - 12}{125} + \frac{V_2}{500} + \frac{V_2 - 12}{250} = 0$$

$$\frac{8 + V_2}{500} + \frac{8 + V_2 - 12}{125} + \frac{V_2}{500} + \frac{V_2 - 12}{250} = 0$$

$$\frac{8}{500} + \frac{V_2}{500} - \frac{4}{125} + \frac{V_2}{125} + \frac{V_2}{500} + \frac{V_2 - 12}{250} = 0$$


$$V_o \left[\frac{1}{500} + \frac{1}{125} + \frac{1}{500} + \frac{1}{250} \right] = \frac{4}{125} + \frac{12}{250} - \frac{8}{500}$$

$$V_o(0.016) = 0.064 \quad \boxed{V_o = 4V}$$

$$V_a = 4V = V_o$$

$$V_b = 12V$$

Using Supernode

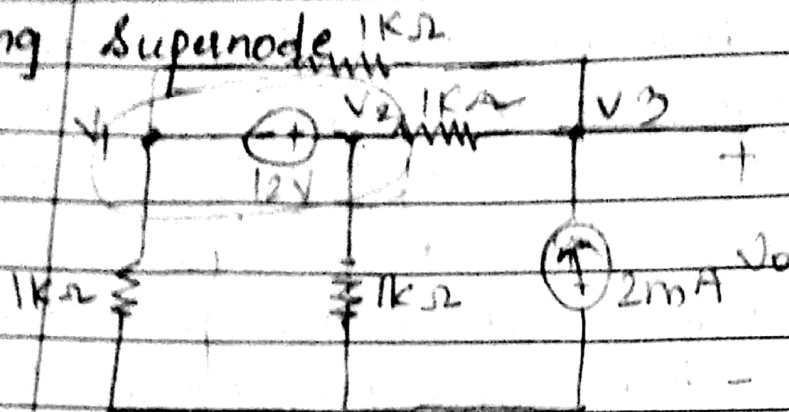

$$-V_1 + V_2 = 12$$

$$V_2 = 12 + V_1$$

$$\frac{V_1}{1k} + \frac{V_1 - V_3}{1k} + \frac{V_2}{1k} + \frac{V_2 - V_3}{1k} = 0$$

$$V_1 + V_1 - V_3 + V_2 + V_2 - V_3 = 0$$

$$2V_1 + 2V_2 - 2V_3 = 0$$

$$V_1 + V_2 - V_3 = 0$$

$$V_1 + 12 + V_1 = V_3$$

$$2V_1 + 12 = V_3$$

$$\frac{V_3 - V_2}{10^3} + \frac{V_3 - V_1}{10^3} = 2 \times 10^{-3}$$

$$2V_3 - V_2 - V_1 = 2 \times 10^{-3} \times 10^3$$

$$2(2V_1 + 12) - 12 - V_1 - V_1 = 2$$

$$4V_1 + 24 - 12 - 2V_1 = 2$$


$$2V_1 + 12 = 2$$

$$2V_1 = -10$$

Determine current i_1 in follⁿ ckt using nodal analysis.

PAGE NO.:

DATE: / /

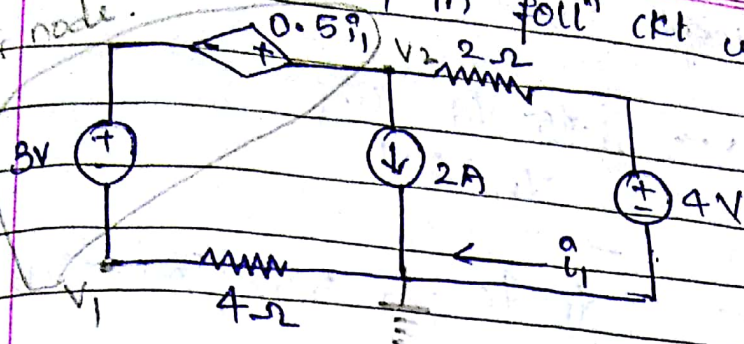

Constraint eqⁿ

$$V_2 - V_1 = 3 + 0.5i_1$$

$$i_1 = \frac{V_2 - 4}{2}$$

$$V_2 - V_1 = 3 + \frac{1}{4}(V_2 - 4)$$

$$V_2 - V_1 = 3 + \frac{V_2}{4} - 1$$

$$V_2 - V_1 = 2 + \frac{V_2}{4}$$

$$\frac{V_2 - 4}{2} = -2$$

$$V_2 - 4 = -4$$

$$V_2 = 0$$

$$i_1 = \frac{0 - 4}{2}$$

Applying KCL at Supernode.

$$\frac{V_1}{4} + \frac{V_2 - 4}{2} = -2$$

$$V_1 + 2V_2 - 8 = -8$$

$$V_1 = -2V_2 = -1.4545V$$

$$V_2 + 2V_2 = 2 + \frac{V_2}{4}$$


$$11V_2 = 8$$

$$V_2 = 8/11$$

$$3V_2 - \frac{V_2}{4} = 2$$

$$i_1 = -1.068A$$

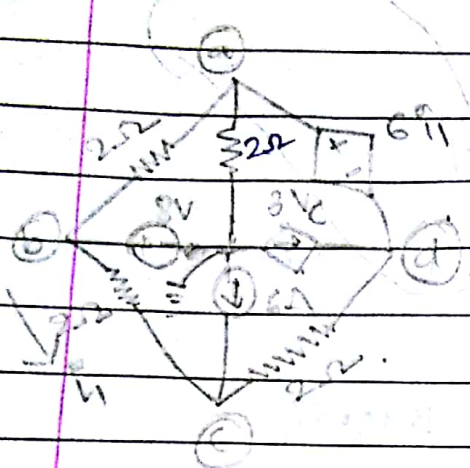⊛ Determine node voltages V_b and V_c in follⁿ ckt.



$$V_a - V_d = 6i_1$$

$$V_b = 8V$$

$$\frac{V_b - V_c}{2} = i_1 \Rightarrow V_c = 2i_1 + V_b$$

KCL at supernode

$$\frac{V_a}{2} + \frac{V_a - V_b}{2} + \frac{V_d - V_c}{2} = 3V_c$$

$$V_a + V_a - V_b + V_d - V_c = 6V_c$$

$$V_d + 2V_a - 8 - V_c = 6V_c$$

$$V_d + 2V_a - 8 = 7V_c$$

$$V_d + 2V_a - 8 = -14i_1 + 7V_b$$

$$V_d + 2V_a - 8 = -14i_1 + 56$$

$$V_d + 2V_a + 14i_1 = 64$$

$$V_d + 2(6i_1 + V_d) + 14i_1 = 64$$

$$V_d + 12i_1 + 2V_d + 14i_1 = 64$$

$$V_d + 26i_1 + 2V_d = 64$$

$$3V_d + 26i_1 = 64$$

At c

$$\frac{V_c - V_b}{2} + \frac{V_c - V_d}{2} = 6$$

$$\frac{V_c - 8}{2} + \frac{V_c - V_d}{2} = 6$$

$$V_c - 8 + V_c - V_d = 12$$

$$2V_c - 8 - V_d = 12$$

$$2V_c - V_d = 20$$

A-B

$$\frac{V_b - V_a}{2} + \frac{V_b - V_c}{2}$$

$$2(-2i_1 + V_b) - V_d = 20$$

$$-4i_1 + 16 - V_d = 20$$

$$-4i_1 - 4 - V_d = 0$$

$$3V_d + 14i_1 = -12$$

$$3V_d + 26i_1 = 64$$

$$+14i_1 = -12$$

$$i_1 = \frac{-12}{14}$$

$$i_1 = 5.42$$

$$3V_d + 26 \times 5.42 = 64$$

$$3V_d = 64 - 140.92$$


$$V_d = -25.54V$$

$$2V_c = 20 + (-25.54)$$

$$2V_c = 20 - 25.54$$

$$V_c = -2.82V$$

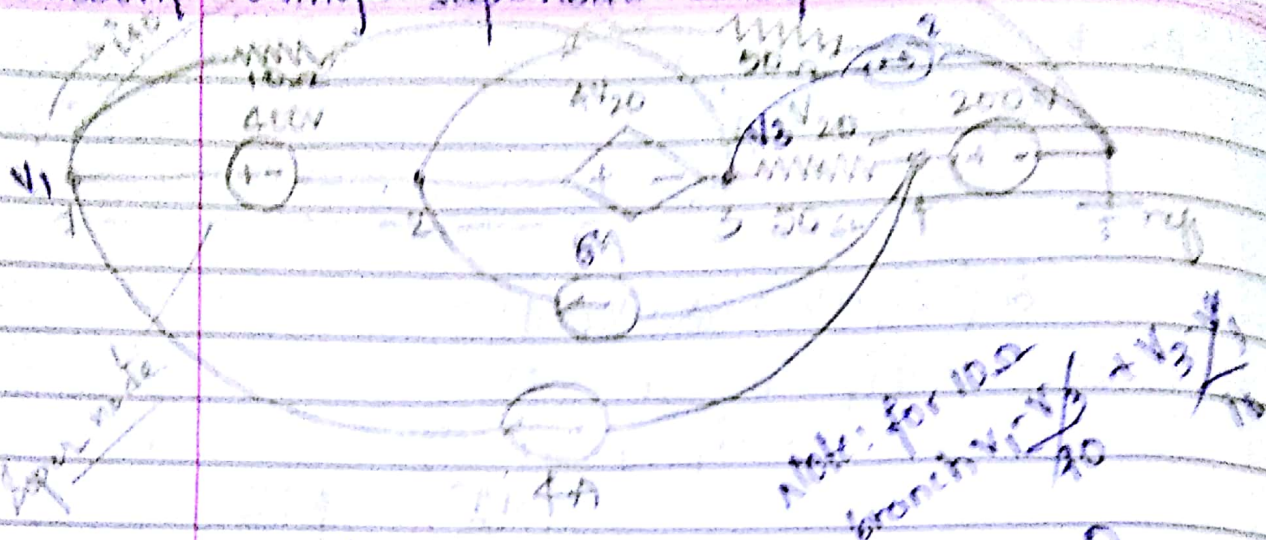Q. Determine the voltage V_{20} and I_{40} in the following network using supernode concept.



$$V_1 - V_3 = 400 + 4V_{20}$$

$$V_4 = 200V$$

$$V_1 - V_3 = 400V$$

$$V_3 - V_4 = V_{20}$$

$$V_3 - V_3 = 4V_{20}$$

$$V_1 - 5V_{20} = 600$$

$$V_3 - 200 = V_{20}$$

$$V_3 = V_{20} + 200$$

Applying KCL at supernode.

$$-6 + \frac{V_1}{40} + 4 + \frac{V_2}{50} + \frac{V_3 - V_4}{20} + 8 = 0$$

$$\frac{V_1}{40} + 12 + \frac{V_2}{50} + \frac{V_{20}}{20} = 0$$

$$\frac{V_1}{40} + 12 + \frac{V_1 - 400}{50} + \frac{V_{20}}{20} = 0$$

$$-6 + V_1(0.045) + 12 - 8 + V_{20}(0.05) = 0$$

$$0.045V_1 + 4 + V_{20}(0.05) = 0$$

$$V_1 + 600 - 5V_{20} = 0$$

$$0.045V_1 + 0.05V_{20} = +21$$

$$V_1 - 5V_{20} = 1600 \times 0.045$$

$$0.045V_1 + 0.05V_{20} = +21$$

$$0.045V_1 - 0.225V_{20} = -21$$

$$0.275V_{20} = 0.39$$

$$V_{20} = 83.63$$

$$V_1 = 145.45V$$

$$V_{20} = -90.9V$$

$$V_2 = 109.1V$$

$$V_2 = -254.5V$$


$$\frac{V_1}{40} = \frac{0}{40}$$

$$\frac{0}{40} = 3.63A$$

Y Δ

(*) Star-Delta-Transformalⁿ:

Δ=Y

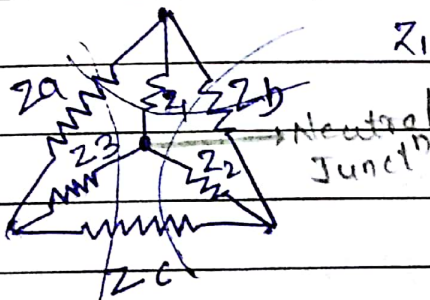

$$Z_1 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

$$Z_1 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$


Y-Δ transformalⁿ

$$Z_A = Z_1 + Z_3 + \frac{Z_1 Z_3}{Z_2}$$


$$Z_B = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$$

$$Z_C = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$$

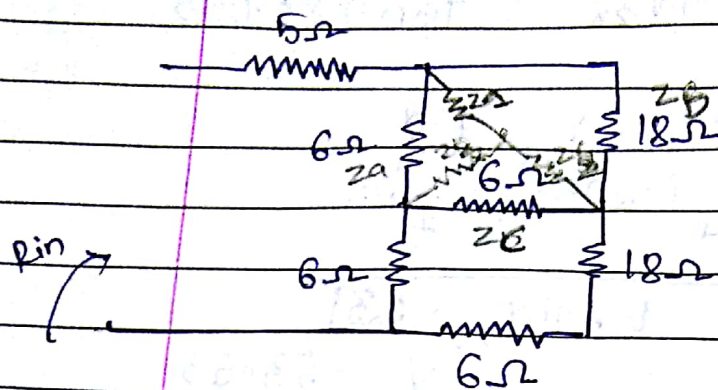⊛ Determine R_{in} using Δ - Y transformⁿ



Δ - Y transformⁿ.

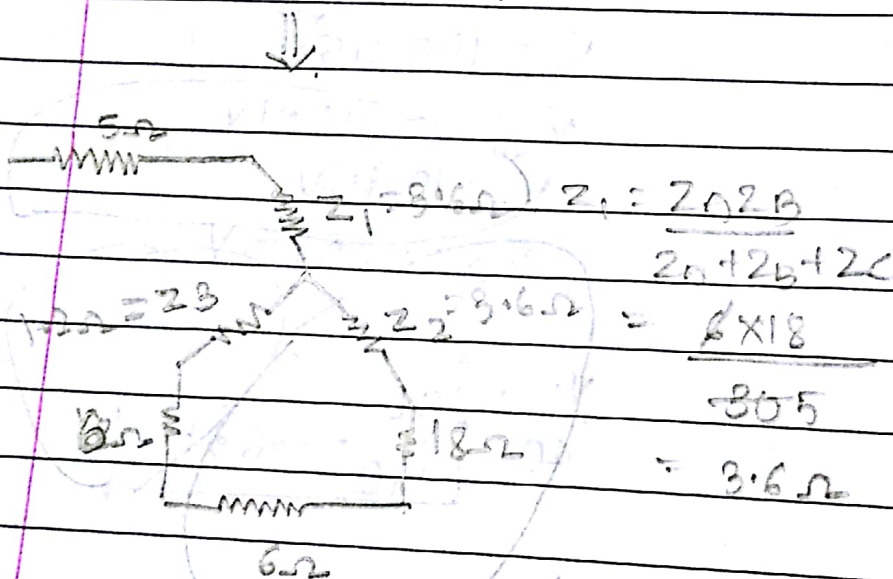

$$Z_1 = 8.16 \Omega$$

$$Z_1 = \frac{2 \times 2 \times 6}{2 + 2 + 6}$$

$$= \frac{24}{10}$$

$$= 2.4 \Omega$$

$$Z_2 = \frac{18 \times 6}{18 + 6 + 6}$$


$$= \frac{108}{30}$$

$$= 3.6 \Omega$$

$$Z_3 = \frac{6 \times 6}{6 + 6 + 6}$$

$$= \frac{36}{18}$$


$$= 2 \Omega$$

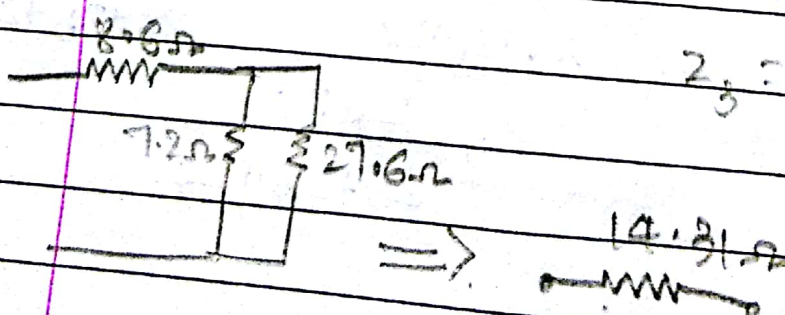

Q. Find bridge determine total resistance seen b/w terminals A and B using Y-Δ transform at?

PAGE NO.:





DATE: / /

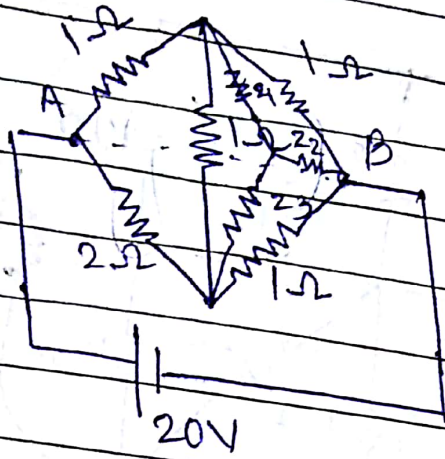

$$Z_1 = \frac{1}{\frac{1}{3}} = \frac{1}{3} \Omega$$

$$Z_2 = \frac{1}{\frac{1}{3}} \Omega$$

$$Z_3 = \frac{1}{\frac{1}{3}} \Omega$$

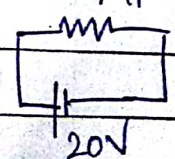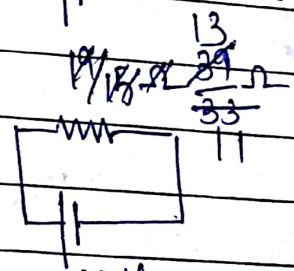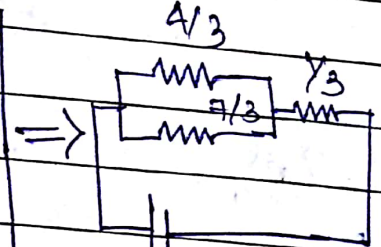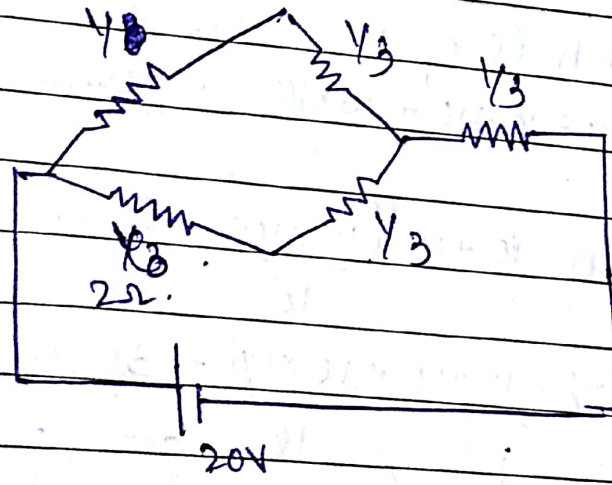

$$\frac{4}{3} \Omega$$

$$\frac{7}{3} \Omega$$

$$\frac{4/3 + 7/3}{1/3} = \frac{11/3}{1/3} = 11 \Omega$$


$$\frac{14}{9} \times \frac{3}{5} = \frac{14}{15}$$

$$\frac{28}{15} \times \frac{3}{11} = \frac{28}{55}$$

$$\frac{28}{33} + \frac{11}{33} = \frac{39}{33} = \frac{13}{11}$$

$$\frac{39}{33}$$

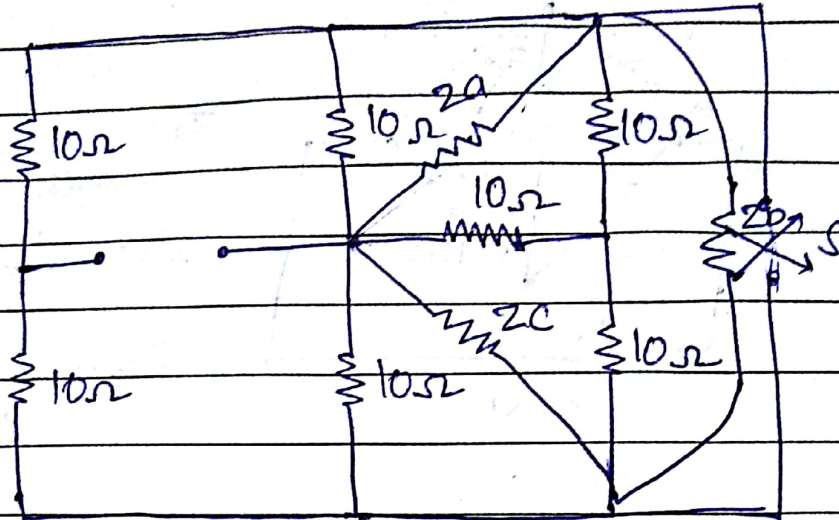- ③ Determine R Equivalent for the follⁿ network when the switch is open and when switch is closed.




④ when switch is open.

$$Z_a = 10 + 10 + \frac{10 \times 10}{10} = 30 \Omega$$

$$Z_b = 10 + 10 + \frac{10 \times 10}{10} = 30 \Omega$$

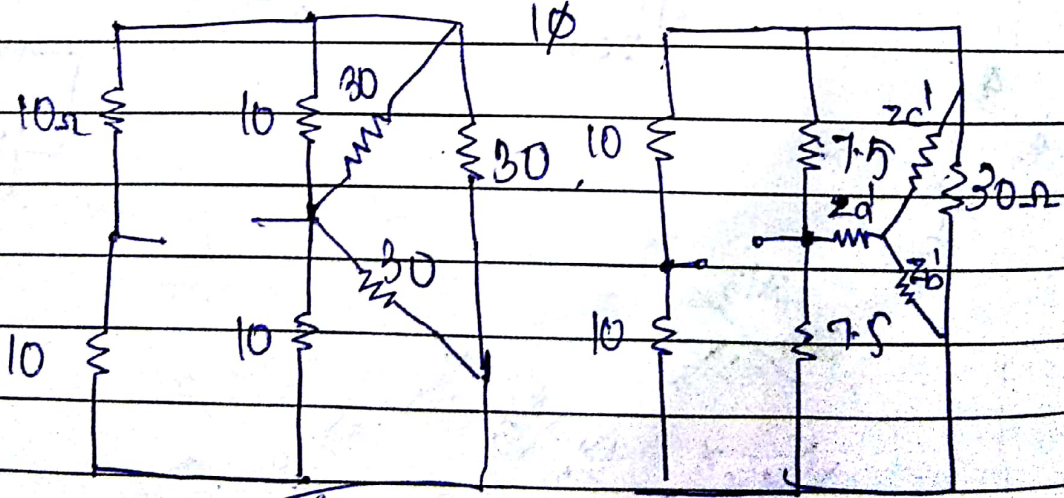
$$Z_c = 10 + 10 + \frac{10 \times 10}{10} = 30 \Omega$$





$$Z_a' = \frac{7.5 \times 7.5}{4.5} = 1.25 \Omega$$

$$Z_b' = \frac{7.5 \times 30}{37.5} = 6 \Omega$$




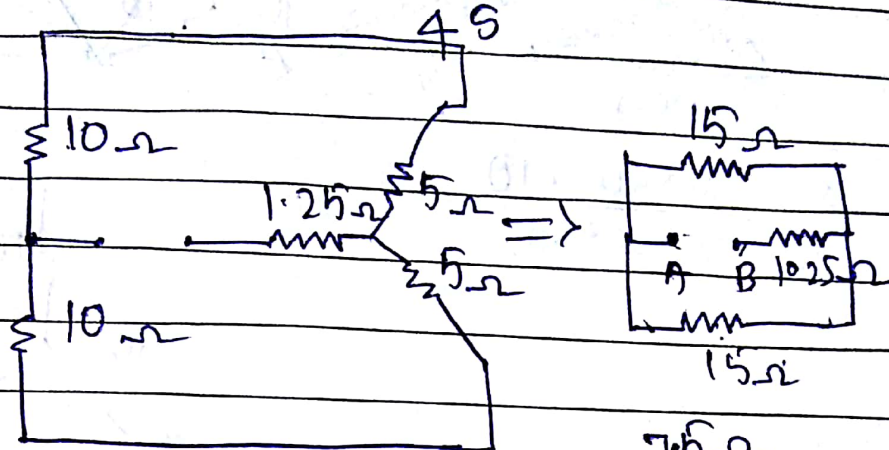
$$Z_c' = \frac{7.5 \times 30}{45} = 5 \Omega$$




$$\frac{15 \times 15}{30}$$

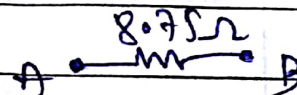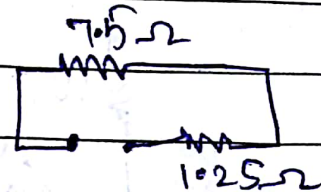





⑥ when switch is closed.

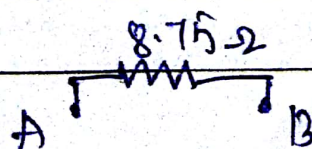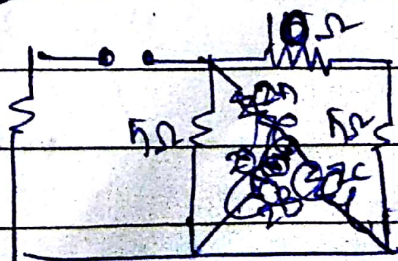
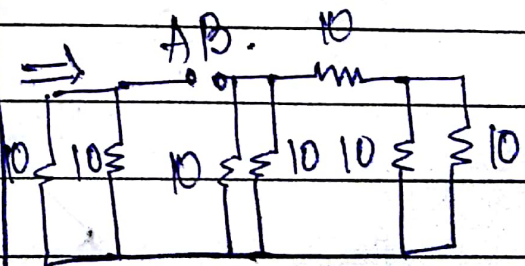
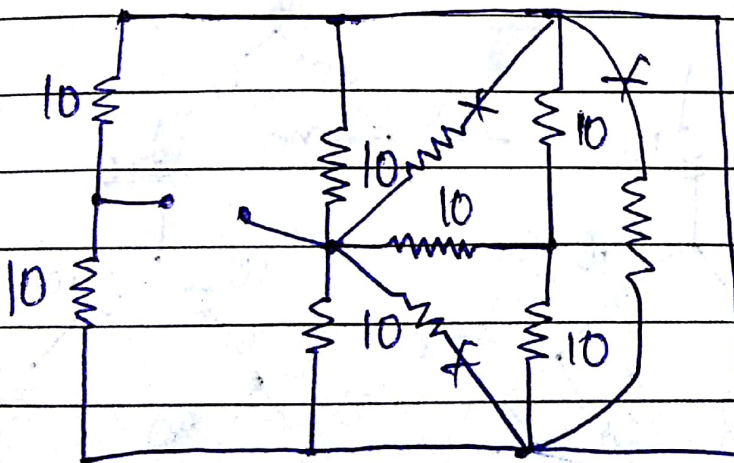


④ Determine R Equivalent for follⁿ Y-Δ

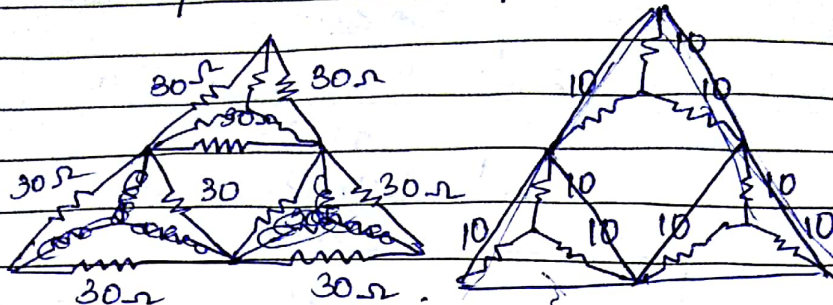
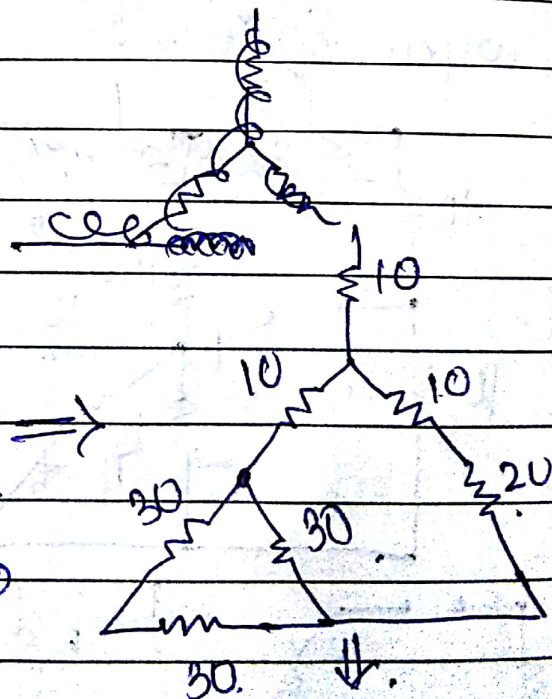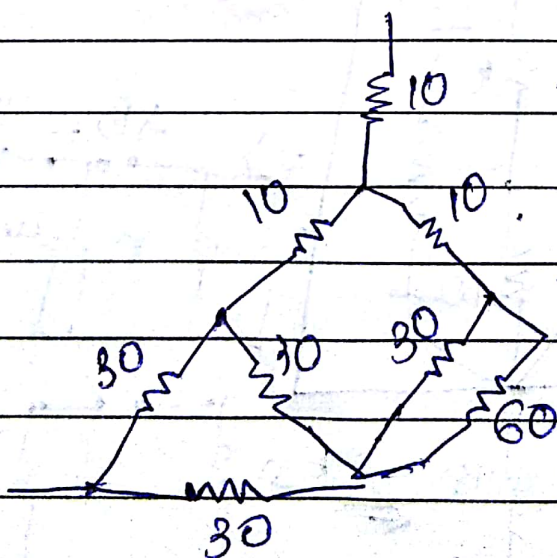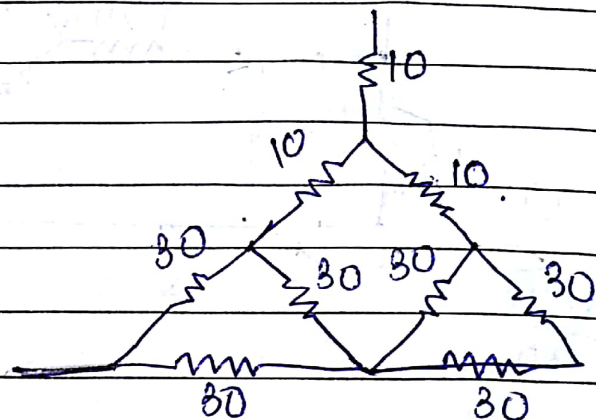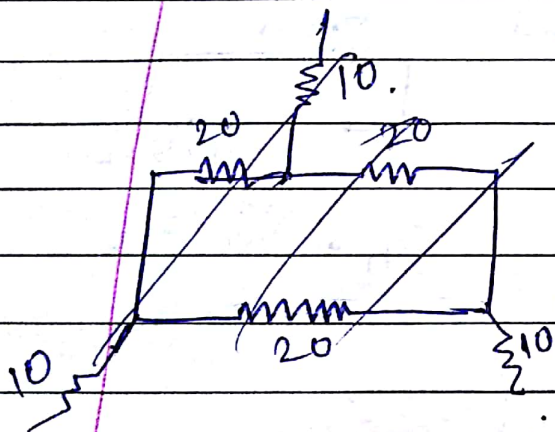
$$2 = \frac{30 \times 30}{30 + 30 + 30} = 10$$



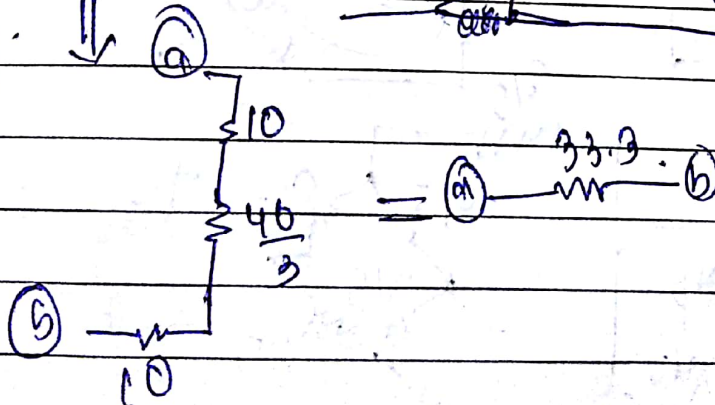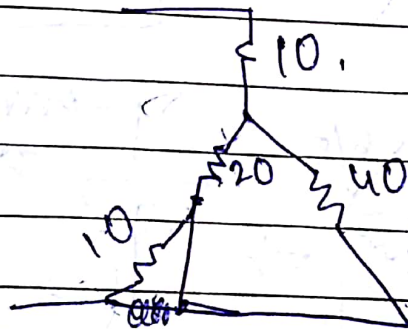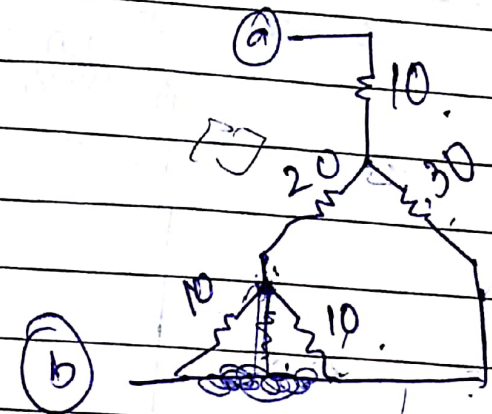

$$\begin{array}{r} 20140 \\ \underline{3} \\ 100 \\ \underline{3} \\ 3 \end{array}$$



$\therefore 33.32$

Det V_s

PAGE NO.:

DATE: / /






(5)

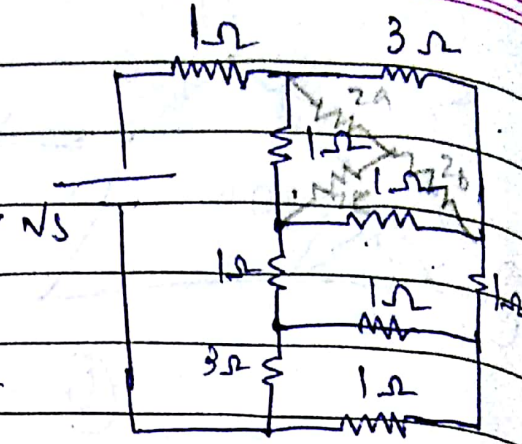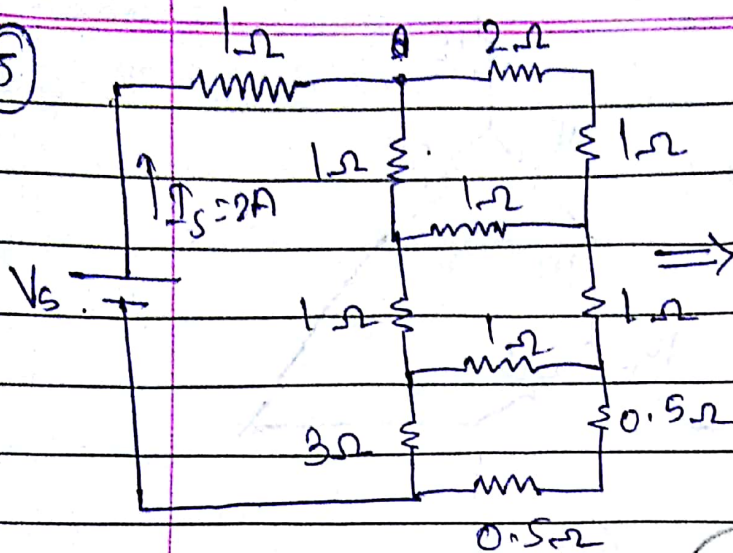


$$Z_a = 9/5$$


$$Z_b = 1/5$$

$$Z_c = 3/5$$

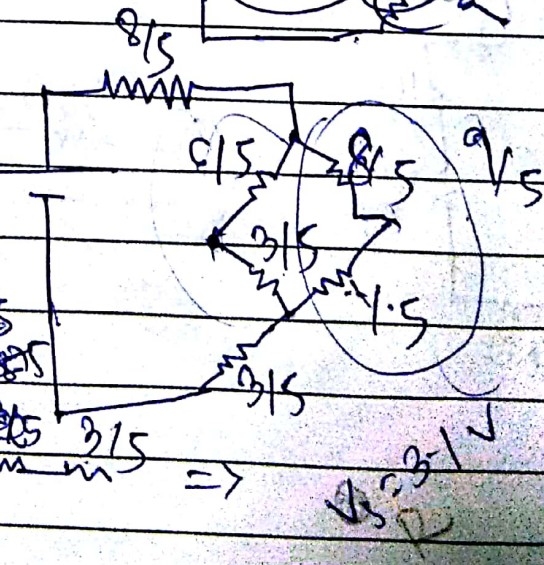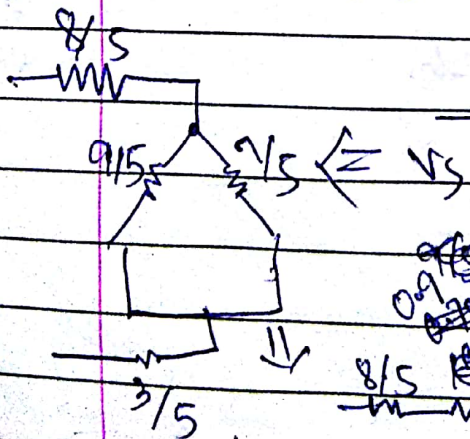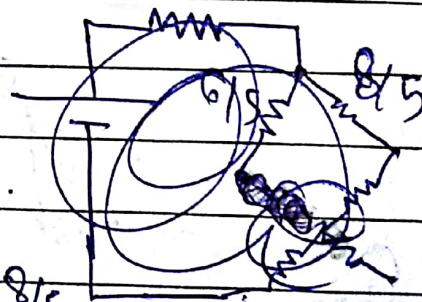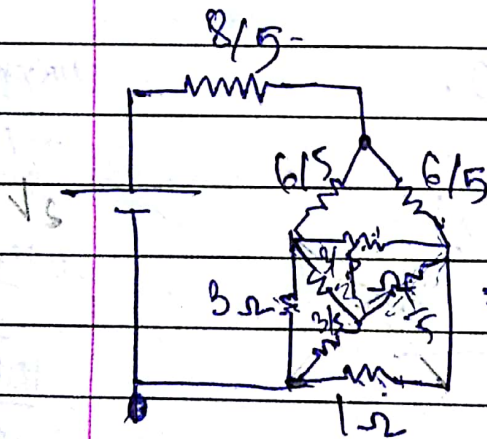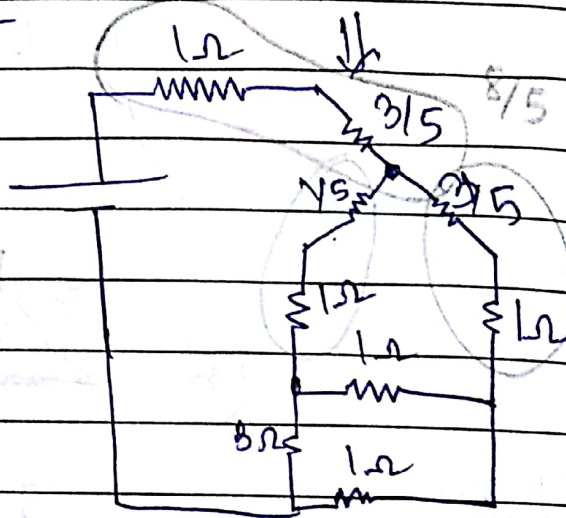

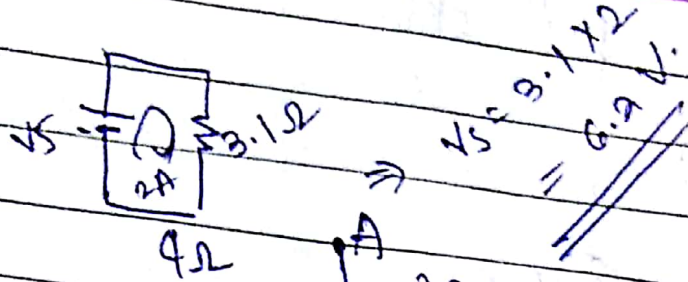

(6)






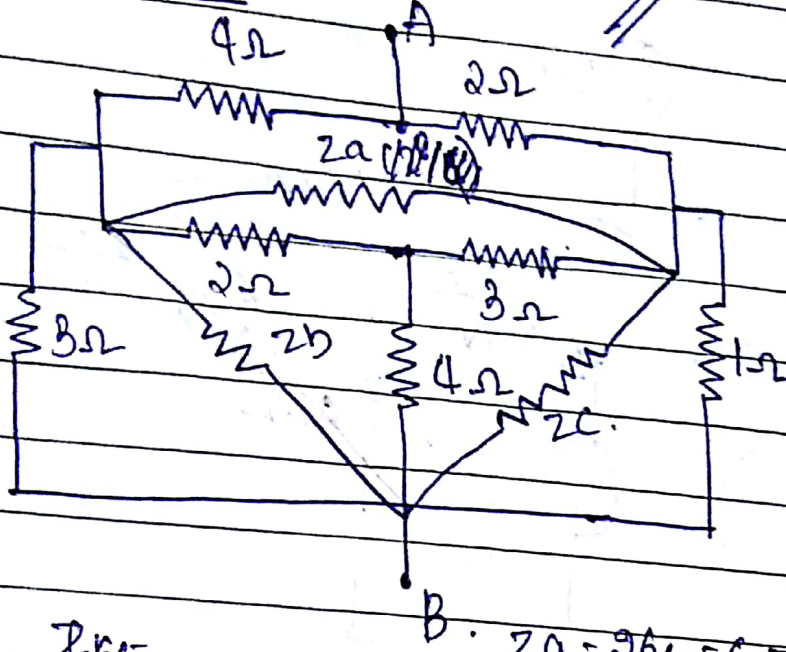


$Z_{AB} =$





$Z_A = 26/4 = 6.5$
 $Z_B = 6 + \frac{8}{1} = 14$

$Z_C = 1 + \frac{12}{3} = 5$
 $Z_D = 6 + \frac{8}{1} = 14$

1.98Ω

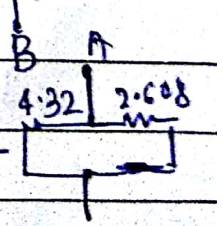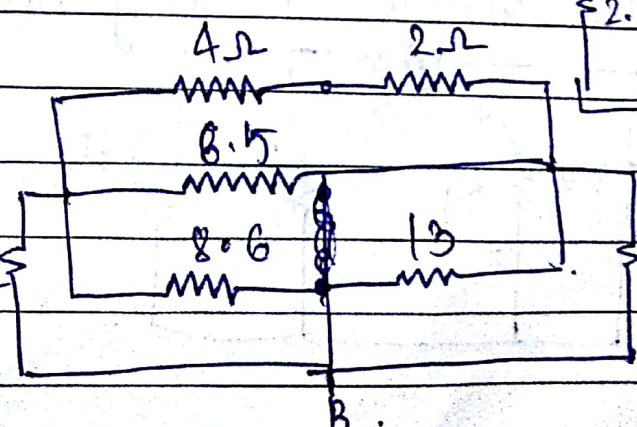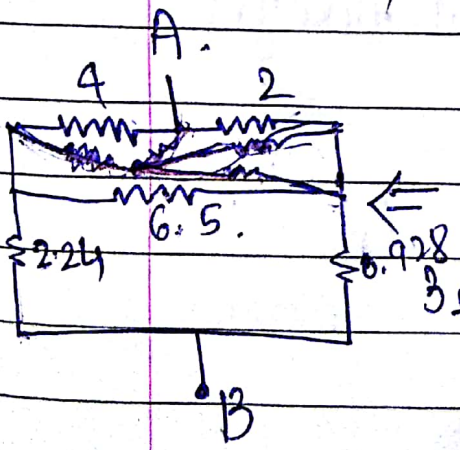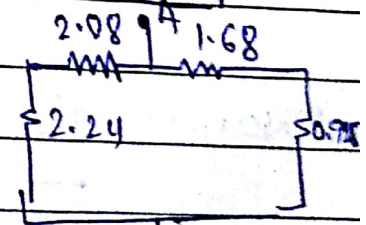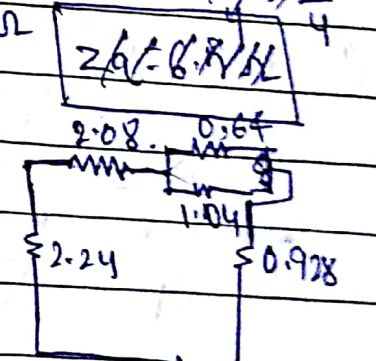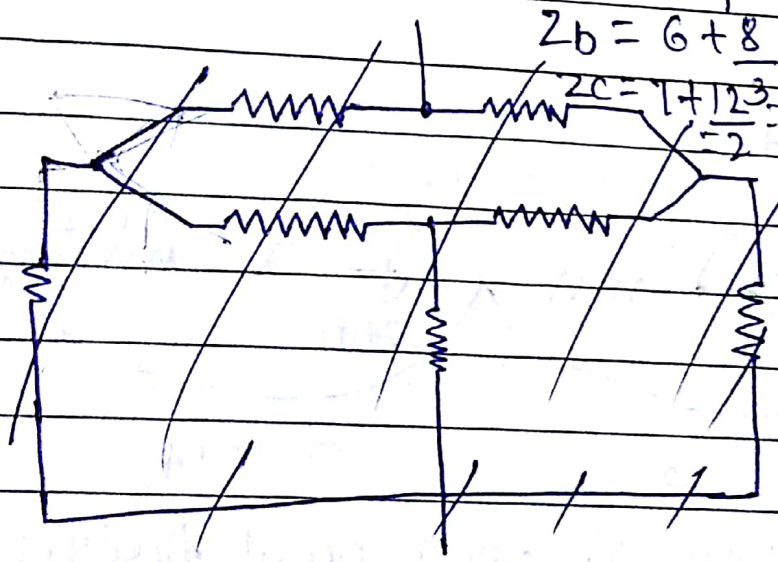

11/10:

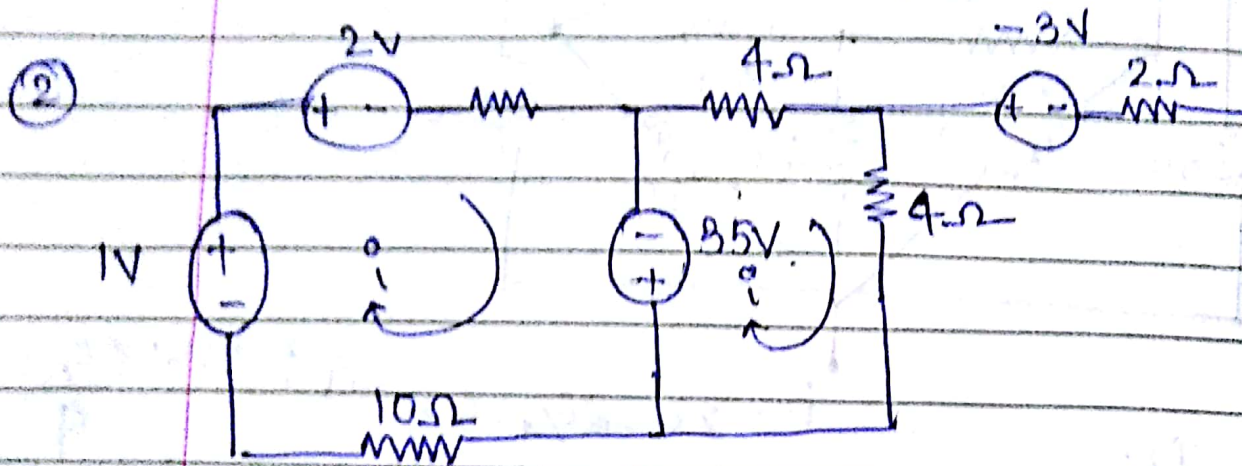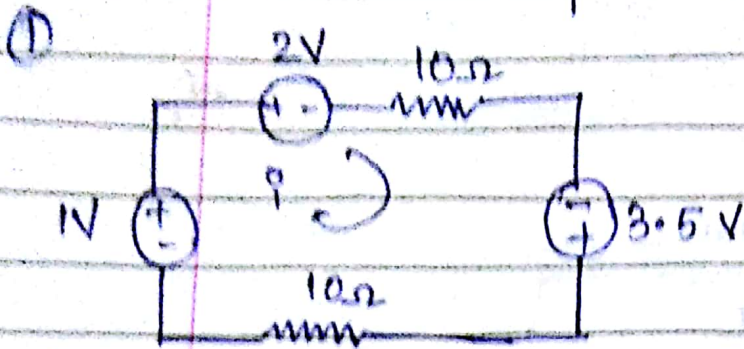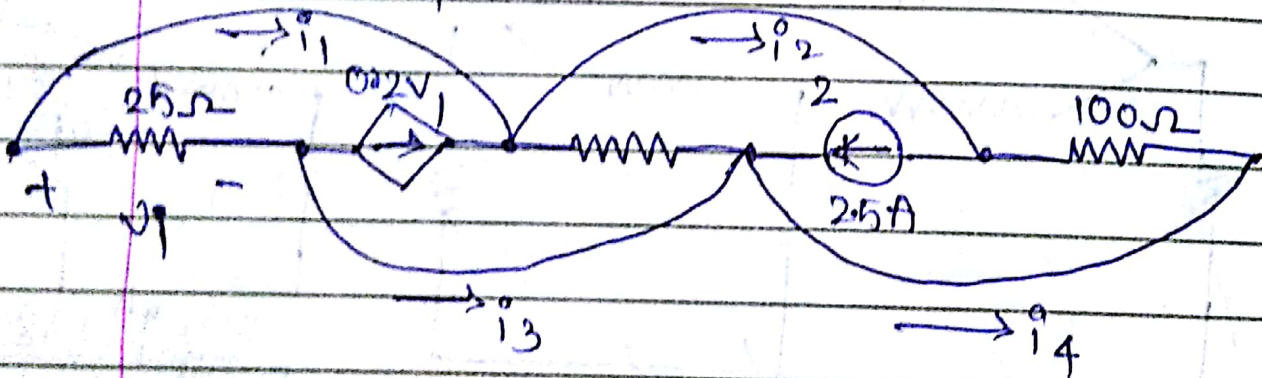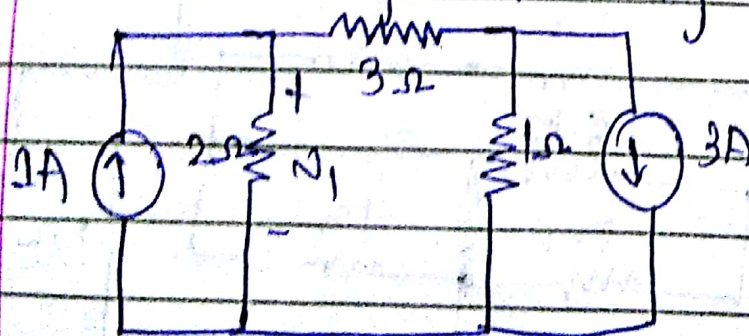Find current i in follⁿ ckt:③ Find i_1, i_2, i_3, i_4 Determine the voltage V_1 using nodal Analysis

For the ckt

- (i) Use nodal Analysis to find V_1 and V_2
 (ii) Compute the power absorbed by the 6Ω resistor

